

## Tutorial support for Assignment 1

The basic equations for answering the questions are all in the lecture notes. The missing ones such as handling circuits with Emitter Resistance are given in Class C lecture slides.

One aspect would be 'where to start':

One way to do this is work backwards – If I asked for AC output for A class, that would be peak values divided by 2 (slide 18 in class A notes)

So find the values that were not given like  $I_c$ . In the question, we have  $R_e$ . So we can get  $I_c$  without know beta value. How? By looking at the voltage into  $R_e$ ... this is where the voltage divider and some circuit analysis comes handy.

Since  $I_e$  is equal to  $I_c$ , we have  $I_c$  now.

Next we need to find  $V_{ceq}$ . To do this, we need to look where  $V_{cc}$  is going.

$V_{cc}$  would be whatever  $V_{ceq}$  is plus voltage drop across  $R_c$  and  $R_e$ . We know  $I_e$  and  $I_c$  now (same), so finding  $V_{ceq}$  is not a problem.

Hope this is helpful.

For C class amp, I have given you all the equations needed in the lecture notes.

For question 3, the simple way is since the voltage divider side circuit is in symmetry, we can just analyse only half of the circuit. So voltage is half.


To find  $R_2$ , we need to know what current is going through the resistors  $r_1$  and  $r_2$ ...

Remember that  $R_2$  need to provide enough voltage to forward bias the BJT....

If you still are wondering how to do, then give it a go and I can provide the solutions once the assignment submitted.

For support, I have included an example:

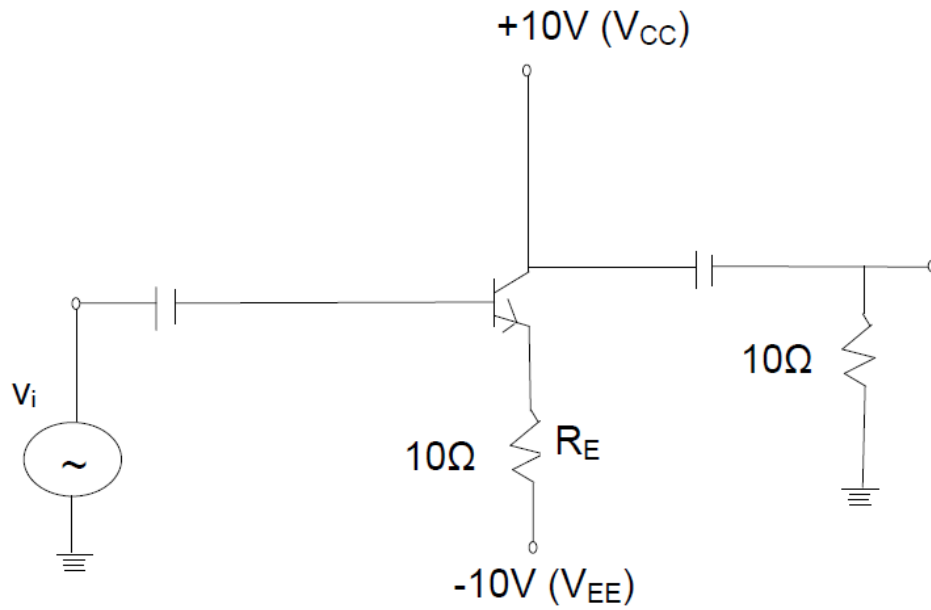Calculate maximum ac output power and efficiency of the amplifier shown in fig.  $V_{BE}$  may be assumed negligibly small.



### Solution:-

The operating point current and voltages in the circuit are:

$$I_{CQ} = I_E = \frac{|V_{EE}|}{R_E} = \frac{10V}{10\Omega} = 1A$$

And,

$$V_{CEQ} = V_{CC} = 10V$$

Therefore, maximum ac output power is,

$$P_{0(max)} = \frac{V_{CEQ} \cdot I_{CQ}}{2} = \frac{10 \times 1}{2} = 5W$$

To calculate the efficiency,  $\eta$ , the dc power drawn by collector-emitter circuit is,

$$\begin{aligned} P_{DC} &= |V_{CC}| + |V_{EE}| I_{CQ} \\ &= (10+10) \times 1 = 20W \end{aligned}$$

Therefore efficiency,

$$\eta = \frac{P_{0(max)}}{P_{DC}} = \frac{5W}{20W} \times 100$$

$$\text{or } \eta = 25\%$$