

ECEN321: Analogue Electronics

Assignment 1: Power Amplifiers - Submission

Daniel Eisen : 300447549

April 27, 2020

Question 1

- I. *An audio amplifier operates in the frequency range of..*
 - a. **20Hz to 20kHz**
- II. *For maximum peak-to-peak output voltage, the Q point should be..*
 - c. **At the centre of the dc load line**
- III. *An amplifier has two load lines because..*
 - d. **All of the above**
- IV. *Push-pull is almost always used with..*
 - b. **Class B**
- V. *Class C amplifiers are almost always..*
 - c. **Tuned RF amplifiers**
- VI. *The input signal of a class C amplifier..*
 - c. **Produces brief pulses of collector current**
- VII. *If $RC=100\Omega$ and $RL=180\Omega$, the ac load resistance equals..*
 - a. **64Ω**
- VIII. *In a class A amplifier, the collector current flows for..*
 - d. **The entire cycle**
- IX. *With class A, the output signal should be..*
 - a. **Unclassified**
- X. *A small quiescent current is necessary with a class AB push-pull amplifier to avoid..*
 - a. **Crossover distortion**

Question 2

- a) In the push push-pull configuration, the base-emitter junctions of the transistors have a potential of $0.7V$. Thus when the input drops below this, at the **crossover** around the zero-point, the output is cut-off. This introduces a flatline distortion between positive and negative half cycles.

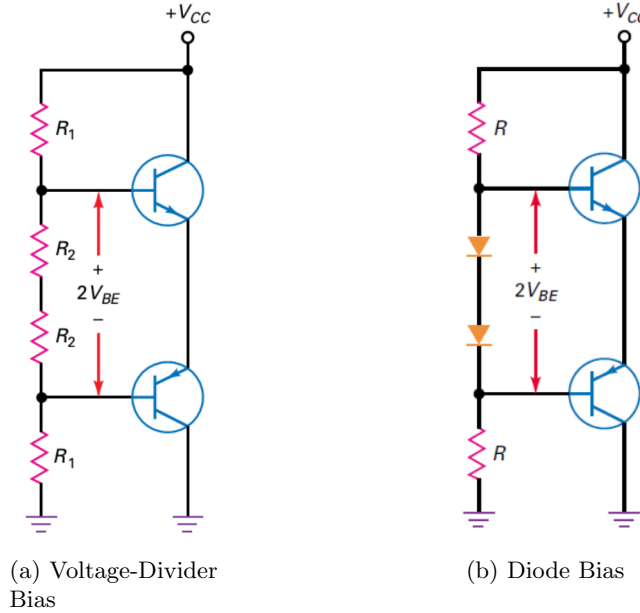


Figure 1: Class B/AB Biasing Configurations

- b) Figure 1a shows a voltage-divider biasing configuration with a summed potential difference of $2V_{BE}$ to ensure the transistors are always on, so as to avoid the crossover distortion. The issue with this is high temperature sensitivity with the ultimate issue being thermal runaway.

Figure 1b shows a diode biasing configuration, this is a way to avoid thermal runaway and still providing the same potential difference. The curves of the compensating diodes must match the V_{BE} curves of the transistors so temperature changes result in an adjusted bias voltage.

Question 3

$$V_{CC} = +20V \quad R_{1,2} = 1k \quad R_C = 50\Omega \quad R_E = 100\Omega \quad R_L = 50\Omega$$

i)

$$\begin{aligned} P_{i(dc)} &= V_{CC} \cdot I_{CQ} \\ V_B &= \frac{R_2}{R_1 + R_2} V_{CC} = \frac{1k}{1k + 1k} 20V = 10V \\ V_E &= V_B - 0.7 = 9.3V \\ I_E &= \frac{V_E}{R_E} = \frac{9.3}{100} = 93mA \approx I_{CQ} \\ \therefore P_{i(dc)} &= 20 \times 93mA = 1.86W \end{aligned}$$

ii)

$$\begin{aligned} P_{o(ac)} &= \frac{V_{CEQ} \cdot I_{CQ}}{2} \\ V_{CEQ} &= V_C - V_E = (V_{CC} - I_C \cdot R_C) - V_E \\ &= (20V - 93mA \times 50\Omega) - 9.3V = 6.05V \\ \therefore P_{o(ac)} &= \frac{6.05V \times 93mA}{2} = 0.28W \end{aligned}$$

iii)

$$\begin{aligned} \% \eta &= \frac{P_{o(ac)}}{P_{i(dc)}} \times 100 \\ &= \frac{0.28}{1.86} \times 100 = 15\% \end{aligned}$$

Question 4

$$V_{CC} = V_{CEQ} = 5V \quad I_{CQ} = 50mA$$

i)

$$\begin{aligned} P_{o(ac \max)} &= \frac{I_{CQ} \cdot V_{CEQ}}{2} \\ &= \frac{50mA \times 5V}{2} = 0.125W \end{aligned}$$

ii)

$$\begin{aligned} P_{i(dc)} &= I_{CQ} \cdot V_{CEQ} \\ &= 50mA \times 5V = 0.25W \end{aligned}$$

iii)

$$\begin{aligned} \% \eta_{\max} &= \frac{P_{o(ac \max)}}{P_{i(dc)}} \times 100 \\ &= \frac{\frac{I_{CQ} \cdot V_{CEQ}}{2}}{I_{CQ} \cdot V_{CEQ}} \times 100 \\ &= \frac{0.125}{0.25} \times 100 = 50\% \end{aligned}$$

Question 5

$$V_{CC} = +30V \quad V_{BE} = 0.7V \quad R_1 = 300\Omega \quad R_L = 16\Omega$$

$$V_{CC} = 2R_1 \cdot I + 2V_{BE}$$

$$30V = 600\Omega \times I + 1.4V$$

$$I = \frac{30V - 1.4V}{600\Omega} = 47.67mA$$

$$R_2 = \frac{V_{BE}}{I} = \frac{0.7V}{47.67mA} = 14.67\Omega$$

Question 6

$$f = 3MHz \quad V_{CC} = 20V \quad V_{CE(sat)} = 0.3V \quad I_P = 500mA$$

i)

$$V_P = V_{CC} - V_{CE(sat)}$$

$$= 20V - 0.3 = 19.7V$$

$$P_O = \frac{V_P^2}{2R_L} = \frac{388.09}{200} = 1.94W$$

$$I_{dc} = \frac{P_O}{V_P} = \frac{1.94}{19.7} = 98.5mA$$

$$P_{dc} = V_{CC} \cdot I_{dc} = 20 \times 98.5 = 1.97W$$

$$\begin{aligned} \% \eta &= \frac{P_O}{P_{dc}} \times 100 = \frac{1.94}{1.97} \times 100 \\ &= 98.5\% \end{aligned}$$

ii)

$$T = \frac{1}{f} = \frac{1}{3 \times 10^6} = 3.33 \times 10^{-7}$$

$$t = \frac{P_O \cdot T}{I_P \cdot V_P} = \frac{1.94 \times 3.33 \times 10^{-7}}{500 \times 19.7} = 6.56 \times 10^{-8}$$

$$\begin{aligned} \phi &= \frac{P_O}{P_{dc}} \times 360 = \frac{6.56 \times 10^{-8}}{3.33 \times 10^{-7}} \times 360 \\ &= 70.92^\circ \end{aligned}$$