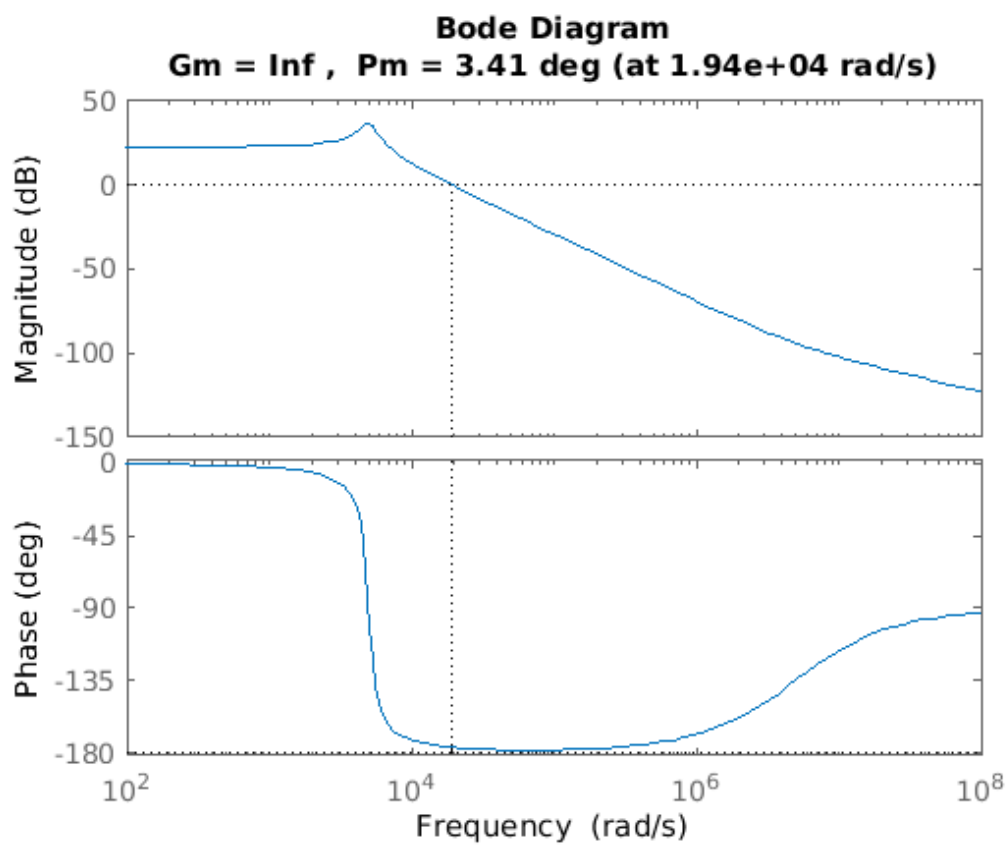


ECEN 405
Lab 6: Power converters
(feedback)
Submission


Daniel Eisen : 300447549
September 22, 2021

1 Buck Converter




2 Controller


3 Controller Bode

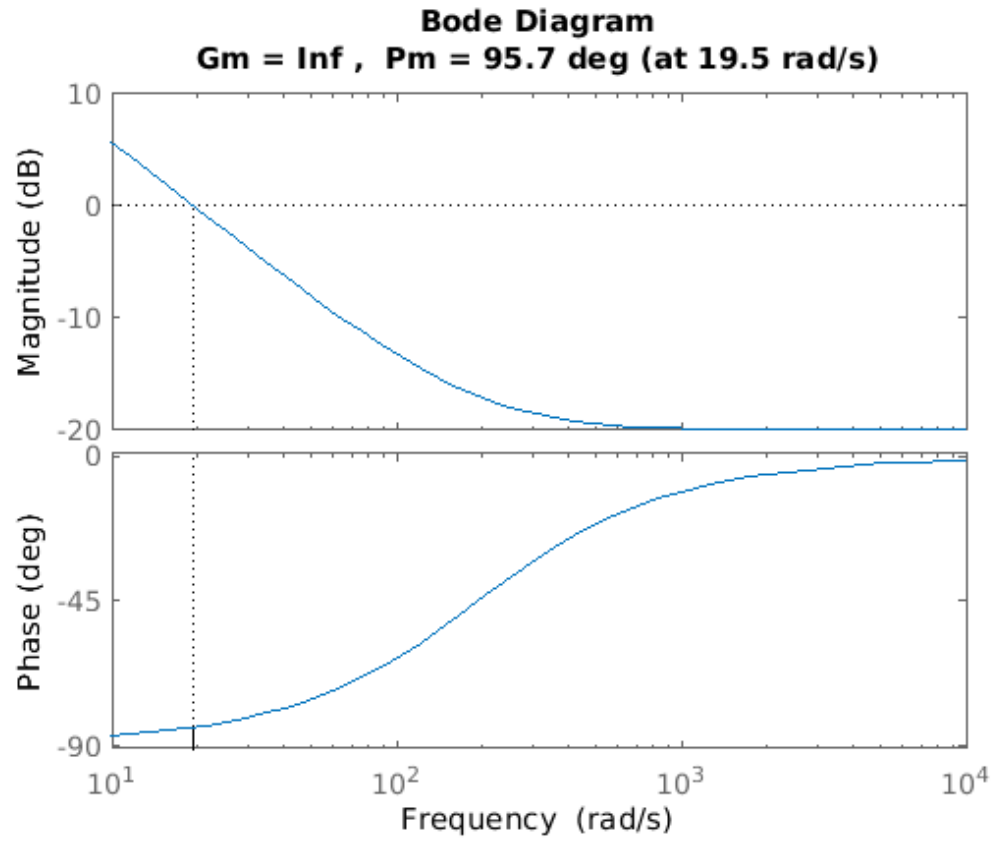

4 Uncontrolled vs Controlled

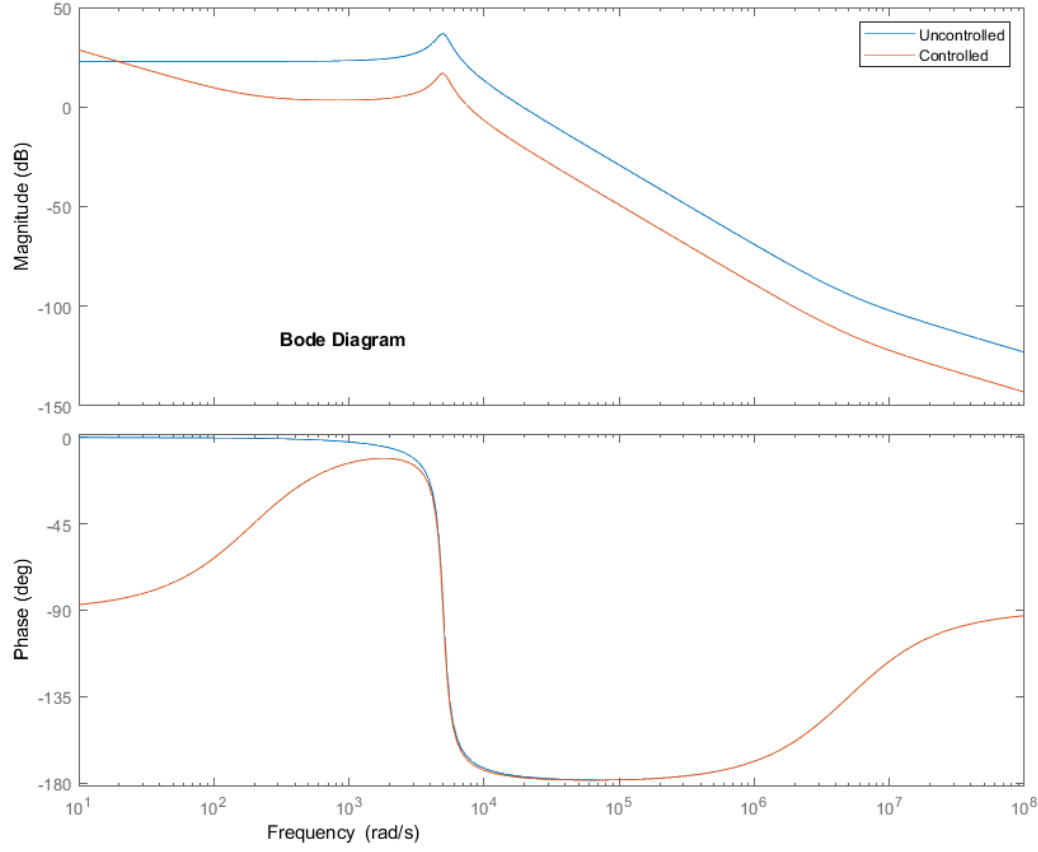

5 Simulink Model

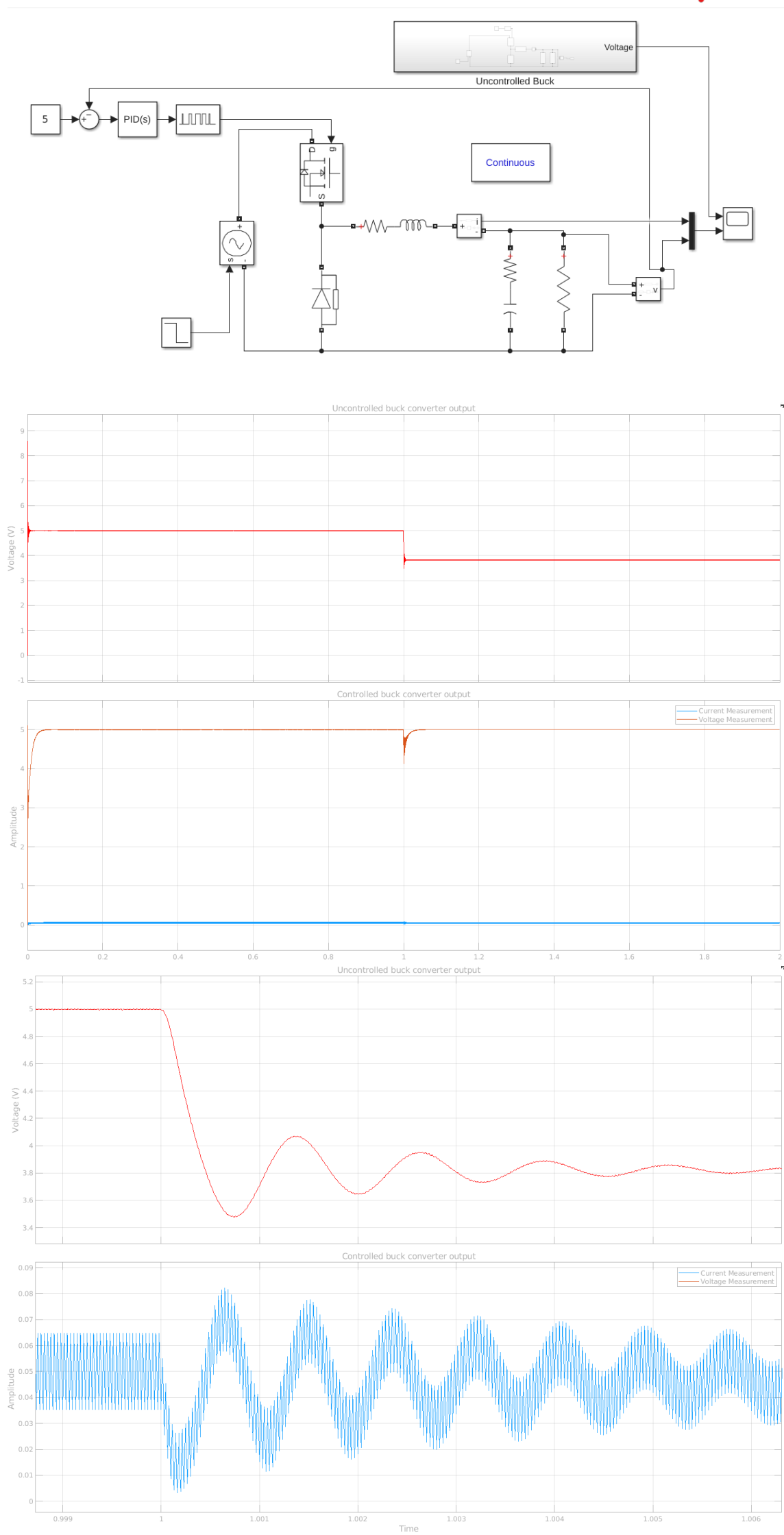

6 Schematic

