

## ECEN203 Analogue Circuits and Systems

### Lab 4

### SPICE 2

## 3. Resonance Frequency.

### 3.1 RLC Transfer Function

$$\begin{aligned}\frac{V_o}{V_i} &= \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \\ &= \frac{R}{R + j\omega L - \frac{j}{\omega C}} \\ \frac{V_o}{V_i} &= \frac{R}{R + j(\omega L - \frac{1}{\omega C})}\end{aligned}$$

### 3.2 Resonance Frequency

$$\text{At resonance } \omega_0 : \omega L = \frac{1}{\omega C}$$


$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 LC = 1$$


$$\omega_0 = \sqrt{\frac{1}{LC}} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}}$$

With  $L = 220\text{mH}$  and  $C = 47\text{nF}$  the expected resonant frequency is :  **$f_0 = 1565\text{Hz}$**

### 3.2 Simulation

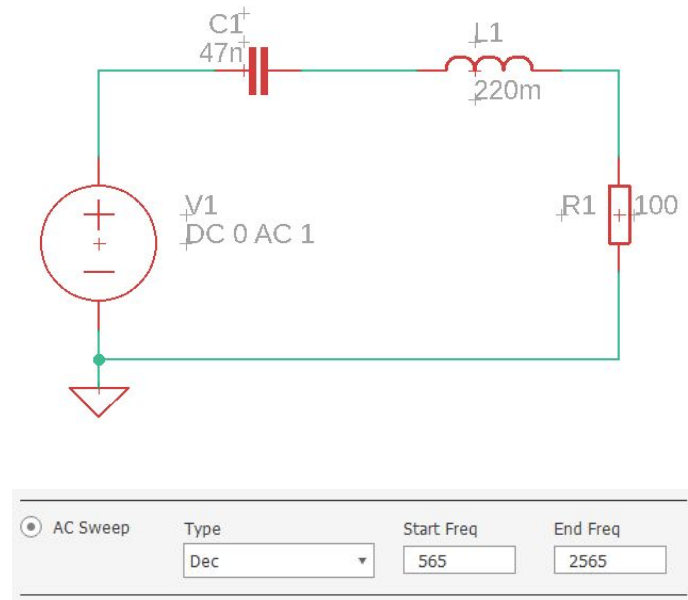


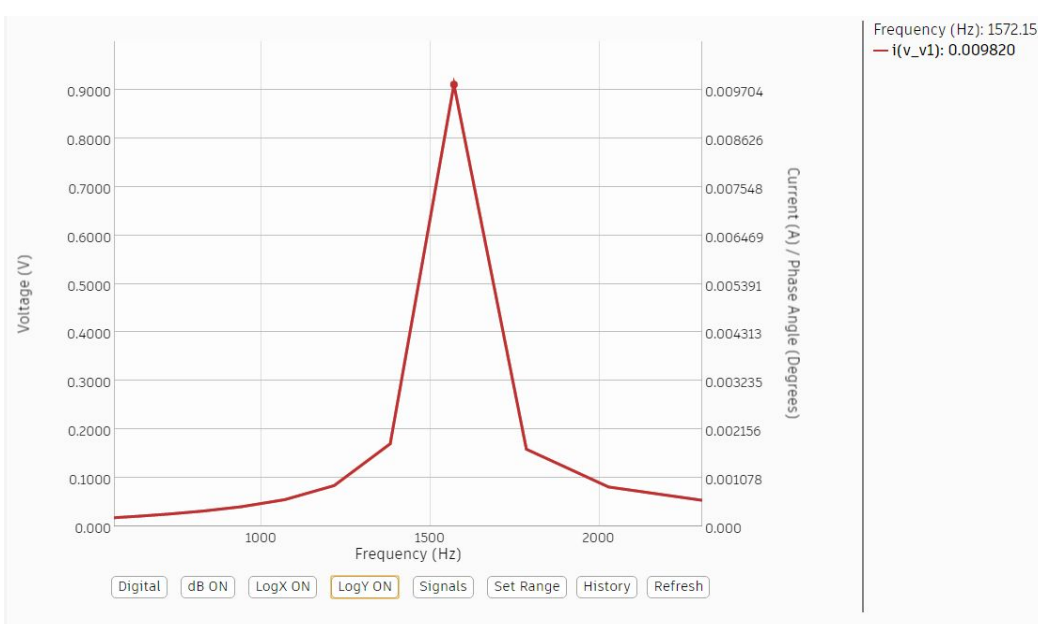Initial circuit setup, AC sweep, enveloped around expected resonance.




6 decades, 3 points per decade.

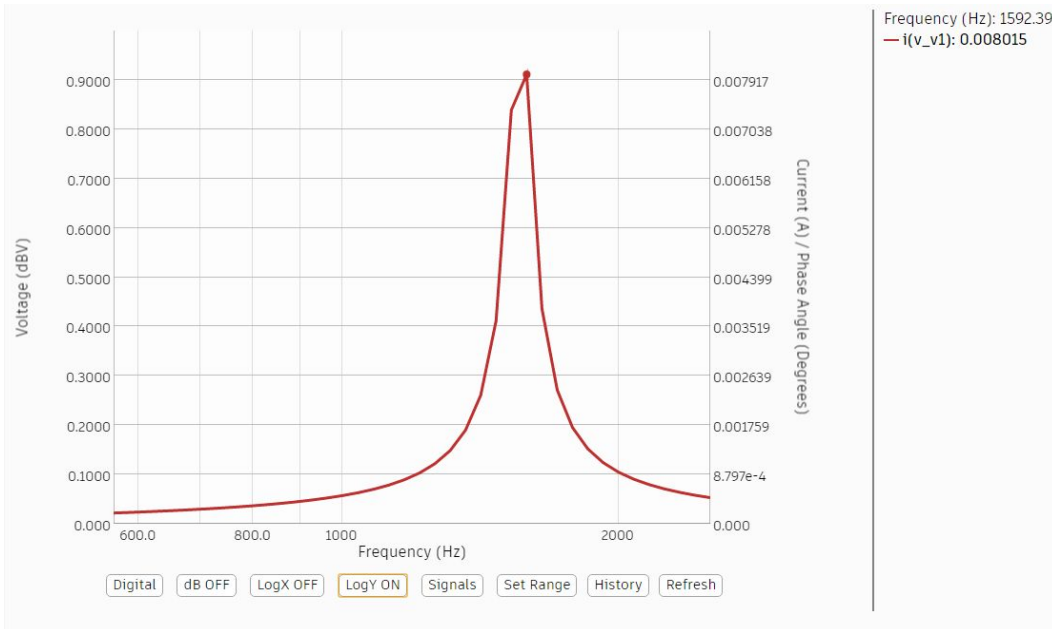Gave  $f_0$  of around 1570, but lacks any detail of surrounding behavior



10 points per decade

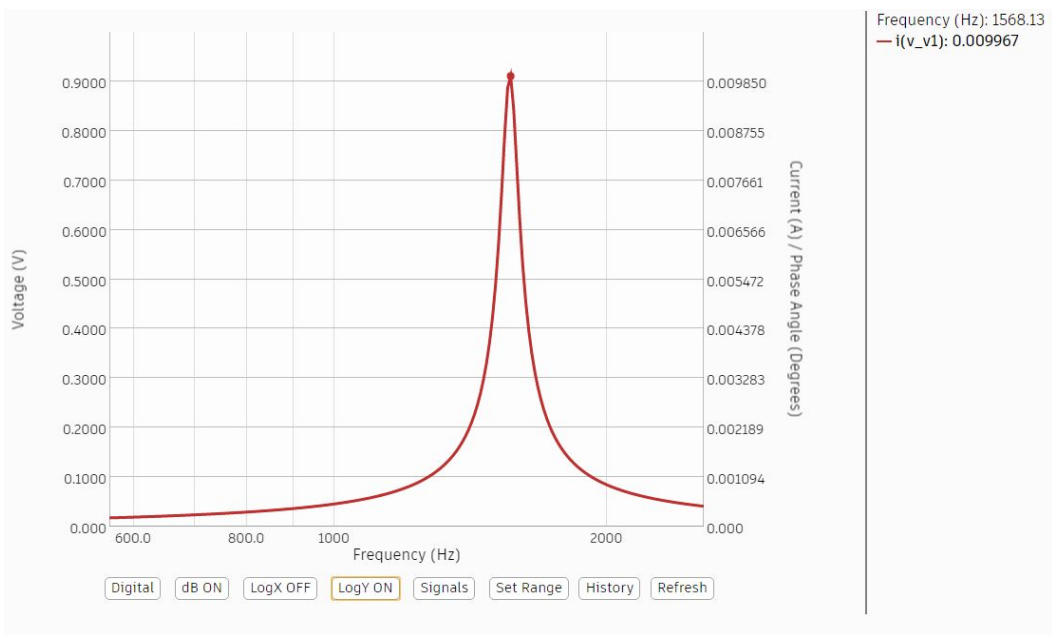Shows more detailed behavior, but sampling overshoots  $f_0$ , showing 1592



50 points per decade, shows good detail and quite accurate  $f_0$ . This sampling rate is adequate but increasing further would be of benefit.

## 4. Q Factor

### 4.1 Quality calc and measurements

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \Rightarrow \frac{1}{100} \sqrt{\frac{220 \times 10^{-3}}{47 \times 10^{-9}}} = 21.6$$

Measured from sim: such that

$$Q = f_0 / f_1 - f_2, \rightarrow Q = 1563 / 1603 - 1527$$

$$Q = 20.56$$

This is quite close, showing adequate representation.


### 4.2 Varying Q $\rightarrow R1$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}, R = \frac{\sqrt{\frac{L}{C}}}{Q}$$


$Q = 0.25$ $R = \frac{\sqrt{\frac{L}{C}}}{0.25}$ $R = 8654\Omega$	$Q = 0.5$ $R = \frac{\sqrt{\frac{L}{C}}}{0.5}$ $R = 4327\Omega$	$Q = 0.707$ $R = \frac{\sqrt{\frac{L}{C}}}{0.707}$ $R = 3060\Omega$	$Q = 1$ $R = \frac{\sqrt{\frac{L}{C}}}{1}$ $R = 2163\Omega$	$Q = 10$ $R = \frac{\sqrt{\frac{L}{C}}}{10}$ $R = 216\Omega$
-------------------------------------------------------------------------	-----------------------------------------------------------------------	---------------------------------------------------------------------------	-------------------------------------------------------------------	--------------------------------------------------------------------

4.2 Transient analysis:  $R = 100$ ;  $\{R\}$  from section above

$R = 100$

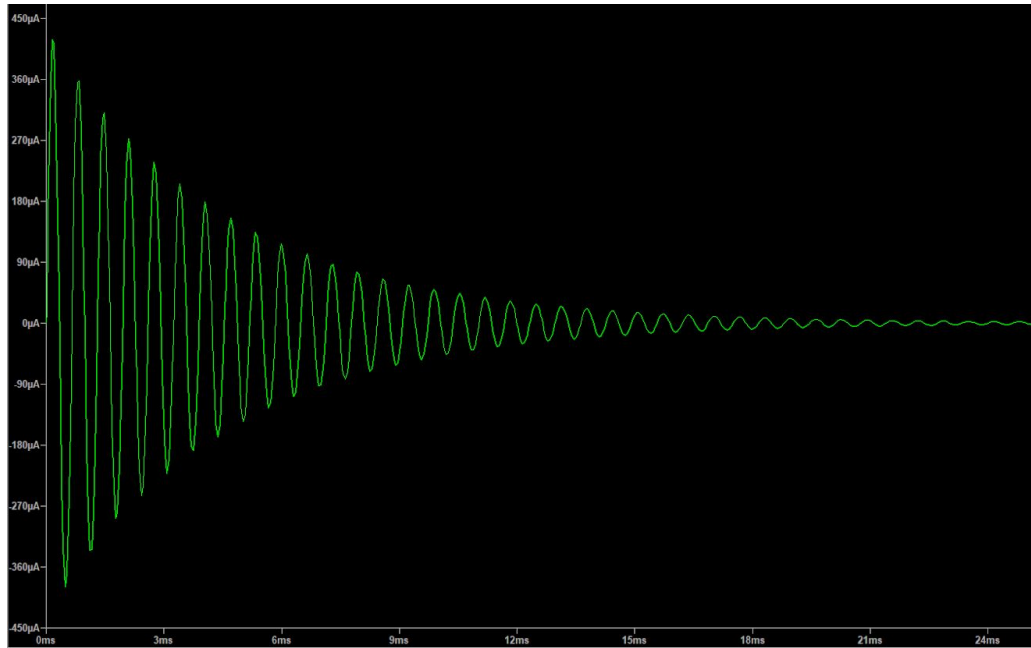

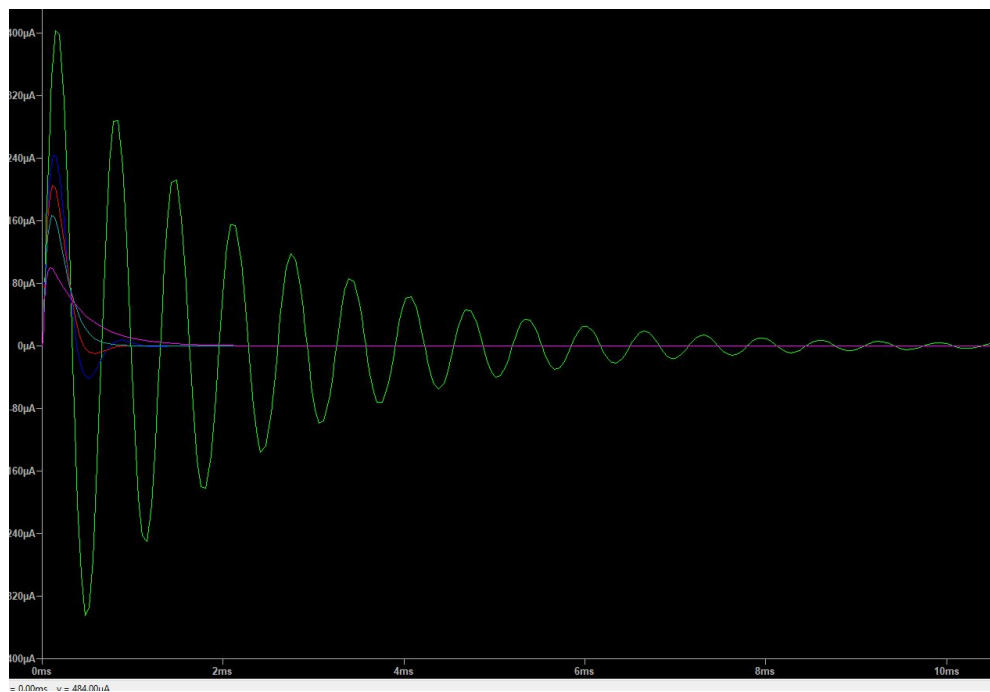Transient R list {8654, 4327, 3060, 2163, 216}



#### 4.3 What is the effect of increasing $Q$ on the transient response of your circuit?

Increasing the  $Q$  value results in less energy dissipation, ie less dampening so circuit oscillations continue for a longer time. With underdamped systems exchanging energy between its reactive components and overdamped systems dissipating that energy too quickly.

Overdamped systems specifically have a higher real energy consumption rate, and asymmetrically approach origin.

Underdamped likewise have a lower rate and oscillate around origin.

#### 5. Parameter sensitivity to component variations in resonant circuits

