

ECEN303 2019 Assignment

Power Amplifiers

Course contribution: 10%

All Questions are worth 10 marks each.

Due: 27 April 1159pm online.

Question 1:

- I. An audio amplifier operates in the frequency range of
 - a. 0 to 20 Hz
 - b. 20 Hz to 2 kHz
 - c. 20 to 20 kHz
 - d. Above 20 kHz
- II. For maximum peak-to-peak output voltage, the Q point should be
 - a. Near saturation
 - b. Near cutoff
 - c. At the centre of the dc load line
 - d. At the centre of the ac load line
- III. An amplifier has two load lines because
 - a. It has ac and dc collector resistances
 - b. It has two equivalent circuits
 - c. DC acts one way and ac acts another
 - d. All of the above
- IV. Push-pull is almost always used with
 - a. Class A
 - b. Class B
 - c. Class C
 - d. All of the above
- V. Class C amplifiers are almost always
 - a. Transformer-coupled between stages
 - b. Operated at audio frequencies
 - c. Tuned RF amplifiers
 - d. Wideband
- VI. The input signal of a class C amplifier
 - a. Is negatively clamped at the base
 - b. Is amplified and inverted
 - c. Produces brief pulses of collector current
 - d. All of the above
- VII. If $R_C = 100\ \Omega$ and $R_L = 180\ \Omega$, the ac load resistance equals
 - a. $64\ \Omega$
 - b. $90\ \Omega$
 - c. $100\ \Omega$
 - d. $180\ \Omega$
- VIII. In a class A amplifier, the collector current flows for
 - a. Less than half the cycle
 - b. Half the cycle
 - c. Less than the whole cycle
 - d. The entire cycle


- IX. With class A, the output signal should be
- Unclipped
 - Clipped on positive voltage peak
 - Clipped on negative voltage peak
 - Clipped on negative current peak
- X. A small quiescent current is necessary with a class AB push-pull amplifier to avoid
- Crossover distortion
 - Destroying the compensating diodes
 - Excessive current drain
 - Loading the driver stage

Question 2:

- With reference to the class B amplifier, explain what is cross over distortion and what causes it.
- Briefly describe, with the aid of diagrams, two methods that can be used to reduce the cross over distortion of a class B amplifier.

Question 3:

Calculate the input power, output power and the efficiency of the following A-class amplifier. Please note that you need to take R_E into account in your calculations.

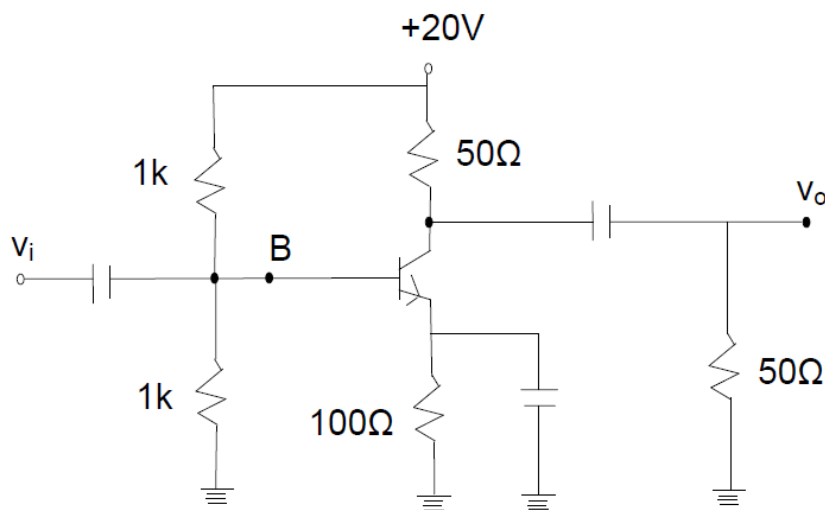


Question 4:

A class A transformer coupled power amplifier has zero signal collector current of 50 mA. If the collector supply voltage is 5 V, find (i) the maximum a.c. power output (ii) the power rating of transistor (iii) the maximum efficiency.

Question 5:

Find the value of resistor R_2 to provide trickle current for distortion free output in the push-pull amplifier shown in the following figure. V_{BE} for each transistor is $0.7V$.

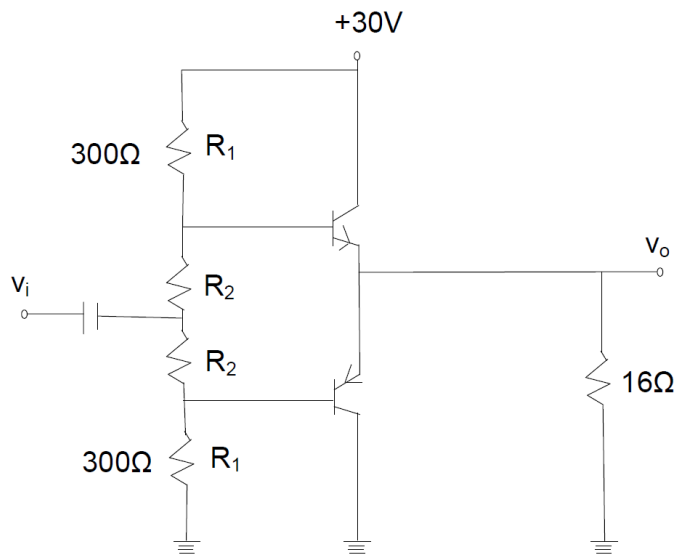

Question 6:

A C-class amplifier shown below, the operating frequency is 3 MHz and $V_{CE(sat)}$ is $0.3V$. Calculate the efficiency. If the peak current is 500 mA , find the conduction angle.

