

# ECEN321: Analogue Electronics

## Assignment 1: Power Amplifiers - Submission

Daniel Eisen : 300447549

April 25, 2020

### Question 1

- I. *An audio amplifier operates in the frequency range of..*
  - a. **20Hz to 20kHz**
- II. *For maximum peak-to-peak output voltage, the Q point should be..*
  - c. **At the centre of the dc load line**
- III. *An amplifier has two load lines because..*
  - d. **All of the above**
- IV. *Push-pull is almost always used with..*
  - b. **Class B**
- V. *Class C amplifiers are almost always..*
  - c. **Tuned RF amplifiers**
- VI. *The input signal of a class C amplifier..*
  - c. **Produces brief pulses of collector current**
- VII. *If  $RC=100\ \Omega$  and  $RL=180\Omega$ , the ac load resistance equals..*
  - $100\Omega$**
- VIII. *In a class A amplifier, the collector current flows for..*
  - d. **The entire cycle**
- IX. *With class A, the output signal should be..*
  - a. **Unclassified**
- X. *A small quiescent current is necessary with a class AB push-pull amplifier to avoid..*
  - a. **Crossover distortion**

### Question 2

- a) In the push push-pull configuration, the base-emitter junctions of the transistors have a potential of 0.7V. Thus when the input drops below this, at the **crossover** around the zero-point, the output is cut-off. This introduces a flatline distortion between positive and negative half cycles.
- b)

### Question 3

$$V_{CC} = +20V \quad R_{1,2} = 1k \quad R_C = 50\Omega \quad R_E = 100\Omega \quad R_L = 50\Omega$$

i)

$$P_{i(dc)} = V_{CC} \cdot I_{CQ}$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{1k}{1k + 1k} 20V = 10V$$

$$V_E = V_B - 0.7 = 9.3V$$

$$I_E = \frac{V_E}{R_E} = \frac{9.3}{100} = 93mA \approx I_{CQ}$$

$$\therefore P_{i(dc)} = 20 \times 93mA = 1.86W$$

ii)

$$P_{o(ac)} = \frac{V_{CEQ} \cdot I_{CQ}}{2}$$

$$\begin{aligned} V_{CEQ} &= V_C - V_E = (V_{CC} - I_C \cdot R_C) - V_E \\ &= (20V - 93mA \times 50\Omega) - 9.3V = 6.05V \end{aligned}$$

$$\therefore P_{o(ac)} = \frac{6.05V \times 93mA}{2} = 0.28W$$

iii)

$$\begin{aligned} \% \eta &= \frac{P_{o(ac)}}{P_{i(dc)}} \times 100 \\ &= \frac{0.28}{1.86} \times 100 = 15\% \end{aligned}$$

### Question 4

$$V_{CC}$$

i)

=

ii)

=

iii)

=

## Question 5

$$V_{CC} = +30V \quad V_{BE} = 0.7V \quad R_1 = 300\Omega \quad R_L = 16\Omega$$

$$V_{CC} = 2R_1 \cdot I + 2V_{BE}$$

$$30V = 600\Omega \times I + 1.4V$$

$$I = \frac{30V - 1.4V}{600\Omega} = 47.67mA$$

$$R_2 = \frac{V_{BE}}{I} = \frac{0.7V}{47.67mA} = 14.67\Omega$$

## Question 6

$$f = 3MHz \quad V_{CC} = 20V \quad V_{CE(sat)} = 0.3V \quad I_P = 500mA$$

i)

$$V_P = V_{CC} - V_{CE(sat)}$$

$$= 20V - 0.3 = 19.7V$$

$$P_O = \frac{V_P^2}{2R_L} = \frac{388.09}{200} = 1.94W$$

$$I_{dc} = \frac{P_O}{V_P} = \frac{1.94}{19.7} = 98.5mA$$

$$P_{dc} = V_{CC} \cdot I_{dc} = 20 \times 98.5 = 1.97W$$

$$\begin{aligned} \% \eta &= \frac{P_O}{P_{dc}} \times 100 = \frac{1.94}{1.97} \times 100 \\ &= 98.5\% \end{aligned}$$

ii)

$$T = \frac{1}{f} = \frac{1}{3 \times 10^6} = 3.33 \times 10^{-7}$$

$$t = \frac{P_O \cdot T}{I_P \cdot V_P} = \frac{1.94 \times 3.33 \times 10^{-7}}{500 \times 19.7} = 6.56 \times 10^{-8}$$

$$\begin{aligned} \phi &= \frac{P_O}{P_{dc}} \times 360 = \frac{6.56 \times 10^{-8}}{3.33 \times 10^{-7}} \times 360 \\ &= 70.92^\circ \end{aligned}$$