

# ECEN 405


## Lab 2: Power converters (Part 1 - Synchronous buck converter) Submission

Daniel Eisen : 300447549

July 26, 2021
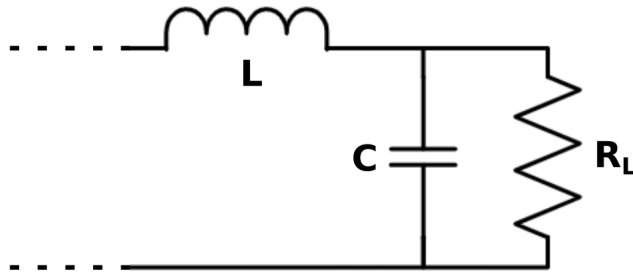
### 1 Output Filter

$V_{in} = 30V$ ,  $V_{out} = 20$ ,  $f_{sw} = 22kHz$ ,  $R_L = 100\Omega$



$$D = \frac{V_{out}}{V_{in}} = 0.66\bar{6}, V_{os} = 0.05V_{out} = 1V$$

$$I_L = \frac{V_{out}}{R_L} 0.2A, I_{ripple} = 0.4I_L = 0.08A, I_{max} = I_L + \frac{I_{ripple}}{2} = 0.24$$

$$L = \frac{V_{out} \cdot (1 - D)}{f_{sw} \cdot I_{ripple}} = 0.00378 = 3.78mH$$

$$C = \frac{I_{max}^2 \cdot L}{(V_o + V_{os})^2 - V_o^2} = 0.0000053215 = 5.32\mu F$$

#### 1.1 Discontinuous Conduction Frequency

$$f_d = \frac{R_L (1 - D)}{2L} = 4400Hz$$

### 2 Deadtime Resistance

From datasheet:

$$R_{DT} = 0 \rightarrow DT = 0.4\mu S$$

$$R_{DT} = 200k \rightarrow DT = 5\mu S$$


$$\frac{\mu S}{k\Omega} = \frac{5 - 0.4}{200} = 0.023$$

$$R_{DT} = \frac{0.5 - 0.4}{0.023} = 4.3478k\Omega$$


Deadtime, in the context on MOSFET gate driving, is the time between 1 FET's gate is switched off and the other is turned on. This prevents the circumstance when (the FETs being in series between V+ and GND without resistance) both FETS are on due to switching delays and causes a short.

### 3 Constant Output

### 4 Waveforms

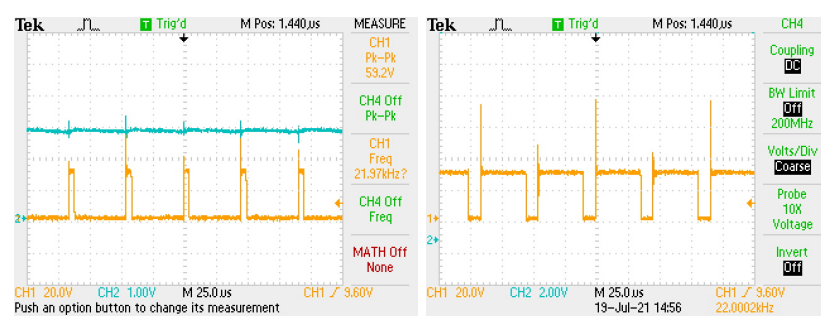

### 5 Efficiency vs Output Current

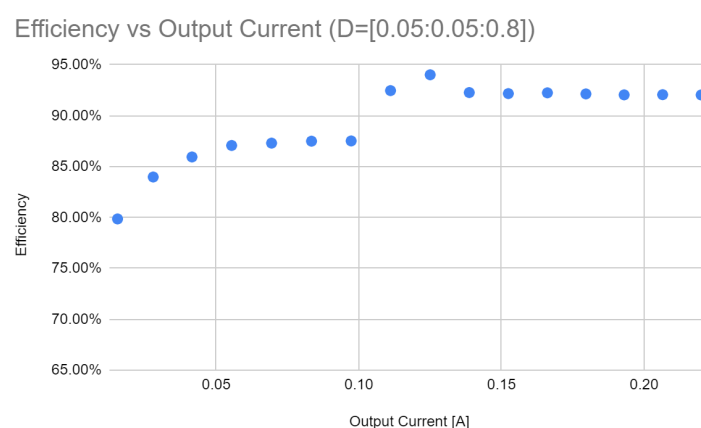

### 6 Bootstrap Circuit