

ECEN203

Analogue Circuits and Systems

Section 1: DC Circuit Analysis

2019



Overview

- Kirchhoff's Laws
- Mesh Analysis
- Nodal Analysis
- Circuit Theorems
- Superposition

Revision

- Voltage, V : energy/charge, (V)
- Current, I : charge/second, (C/s)
- Charge measured in Coulombs (C) $-1C = \text{charge on } 6.241509 \times 10^{18} \text{ electrons}$


Series and Parallel Resistances

- Ohm's Law: $v = iR$
- Power: $P = vi = i^2R = V^2/R$ (W or J/s)
- Series Resistance: $R_S = \sum_i R_i$ ($R_S > R_i$)
- Parallel Resistance: $\frac{1}{R_P} = \sum_i \frac{1}{R_i}$ ($R_P < R_i$)
- Two parallel resistances: $R_P = \frac{R_1 R_2}{R_1 + R_2}$

Conductance

- $G = \frac{1}{R}$
- Series conductances: $\frac{1}{G_S} = \sum_i \frac{1}{G_i}$
- Parallel conductances: $G_P = \sum_i G_i$

Revision - Find R_{TOT} , P_{TOT}

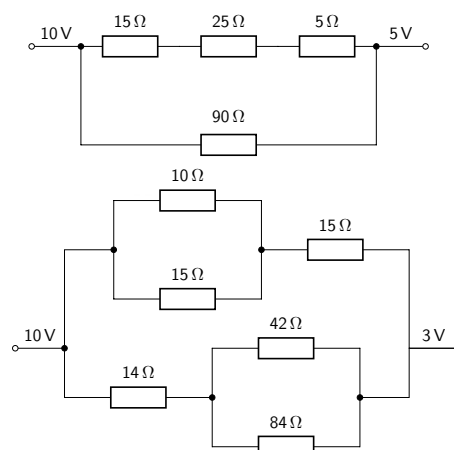

?

$$\begin{aligned}\nabla \times \mathbf{E} &= -\frac{\partial \mathbf{B}}{\partial t} \\ \nabla \times \mathbf{H} &= \mathbf{J} + \frac{\partial \mathbf{D}}{\partial t} \\ \nabla \cdot \mathbf{D} &= \rho \\ \nabla \cdot \mathbf{B} &= 0\end{aligned}$$

Maxwell's Equations



$$\oint_C \mathbf{E} \cdot d\ell = -\frac{d\Phi}{dt}$$

Faraday's Law

$$\oint_C \mathbf{H} \cdot d\ell = I + \int \frac{\partial \mathbf{D}}{\partial t} \cdot d\mathbf{s}$$

Ampère's Law

$$\oint_S \mathbf{D} \cdot d\mathbf{s} = Q$$


Gauss' Law

$$\oint_S \mathbf{B} \cdot d\mathbf{s} = 0$$

No magnetic monopole


Kirchhoff's Current Law

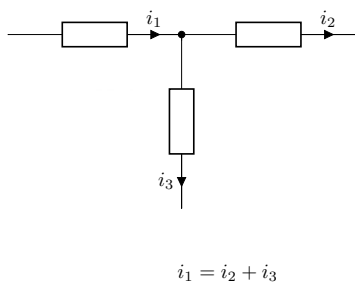- Current Law (KCL): \sum currents in = \sum currents out
- OR (if we label all currents as inwards or outwards) \sum currents = 0



Kirchhoff's Voltage Law

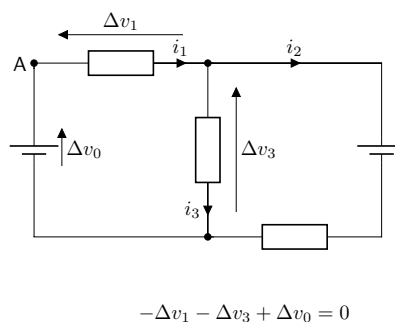- Voltage Law (KVL): \sum voltages in a loop = 0




Kirchhoff's Laws

- Why do Kirchhoff's Laws help us to find currents in a circuit?
- For m currents & n junctions:
 - KVL produces $m - n + 1$ independent equations
 - KCL produces $n - 1$ independent equations
- Total m equations for m unknown currents
- In practice we always need far fewer than this


KVL Polarity: Resistor

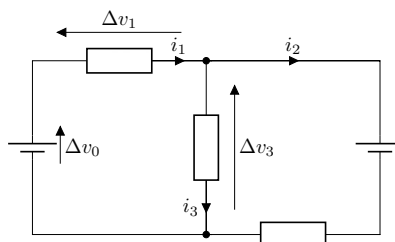- Loop traversing a resistor:
 - In *same* direction as current: $\Delta v = -iR$
 - In *opposite* direction to current: $\Delta v = +iR$



KVL Polarity: Voltage Source

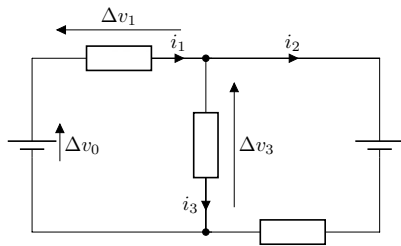
- Loop traversing a voltage source:
 - from -ve to +ve: $\Delta v > 0$
 - from +ve to -ve: $\Delta v < 0$



KVL Polarity: Negatives


- If the solved i is -ve, the actual current is in the opposite direction to the initial arrow
- If the solved v is -ve, the actual voltage is in the opposite direction to the initial arrow

KVL+KCL Example: Find i_1 , i_2 & i_3

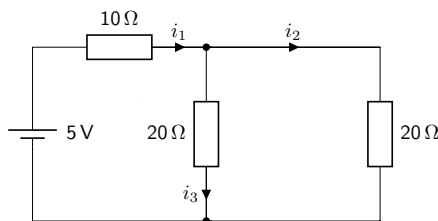


KVL+KCL Example 2

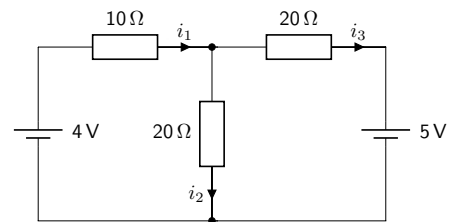- Find the currents in each of the three resistors
- Find the power delivered by each source and dissipated by each resistor




KVL+KCL Example 3

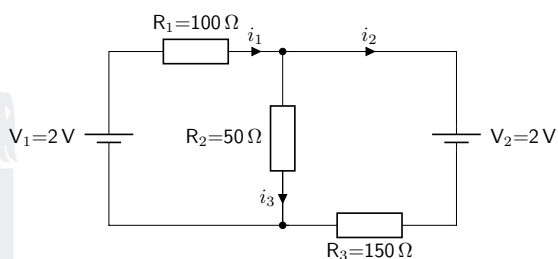

- $n = 2$ junctions: $n - 1$ eqns
- $m = 3$ currents, $m - n + 1$ eqns


A better way...

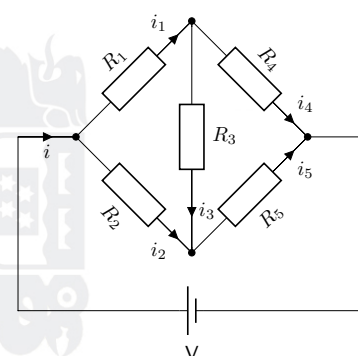- Using KCL & KVL to find currents:
- 6 equations, 6 unknowns




4 junctions give 3 equations:
 $i_1 = i_3 + i_4$
 $i_2 + i_3 = i_5$
 $i = i_4 + i_5 = i_1 + i_2$
 Loops give 3 equations:
 lower: $V - i_2 R_2 - i_5 R_5 = 0$
 left: $-i_1 R_1 - i_3 R_3 + i_2 R_2 = 0$
 right: $i_3 R_3 - i_4 R_4 + i_5 R_5 = 0$

Mesh Analysis (I)

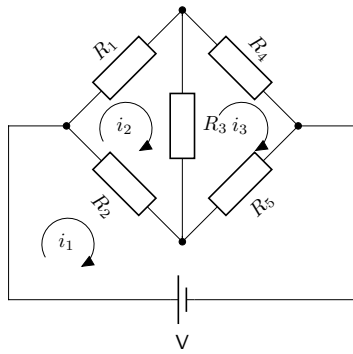


- Assign 1 current/loop
- Apply KVL around each loop, taking into account *all* currents

Mesh Analysis (II)

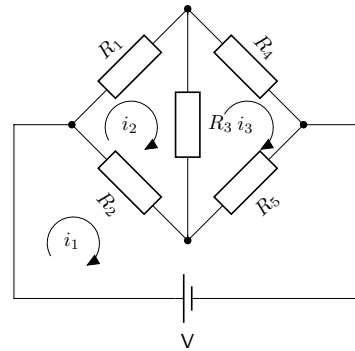


- 3 equations in 3 unknowns
- Junction equations (KCL) are "hidden"
- Actual current is sum of nominal currents, e.g., i in R_2 is $i_1 - i_2$.

Mesh Analysis (III)

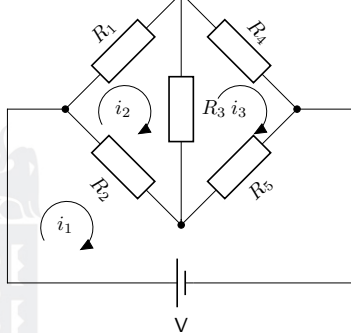

- Lower loop: $V - R_2(i_1 - i_2) - R_5(i_1 - i_3) = 0$
 $V - i_1(R_2 + R_5) + i_2R_2 + i_3R_5 = 0$
- LH loop: $-R_1i_2 - R_3(i_2 - i_3) - R_2(i_2 - i_1) = 0$
 $i_1R_2 - i_2(R_1 + R_2 + R_3) + i_3R_3 = 0$
- RH loop: $-R_3(i_3 - i_2) - R_4i_3 - R_5(i_3 - i_1) = 0$
 $i_1R_5 + i_2R_3 - i_3(R_3 + R_4 + R_5) = 0$

Mesh Analysis (IV)

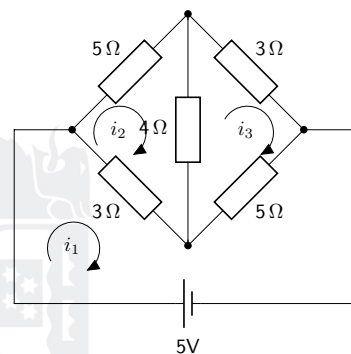


- Lower loop: $5 - i_1(3 + 5) + i_23 + i_35 = 0$
- LH loop: $i_13 - i_2(5 + 4 + 3) + i_34 = 0$
- RH loop: $i_15 + i_24 - i_3(4 + 3 + 5) = 0$

$$\begin{bmatrix} -8 & 3 & 5 \\ 3 & -12 & 4 \\ 5 & 4 & -12 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -5 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{matrix} i_1 = 1.290 \text{ A} \\ i_2 = 0.564 \text{ A} \\ i_3 = 0.726 \text{ A} \end{matrix}$$

Mesh Analysis: Example

- Find i through 4Ω resistor

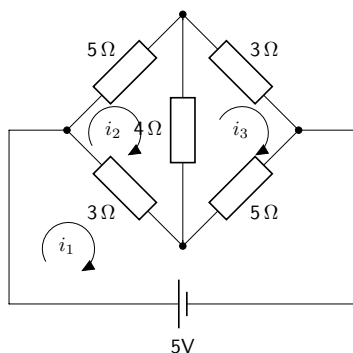


$$i_3 - i_2 = 0.726 - 0.565 = 0.161 \text{ A in the direction of } i_3 \text{ (upwards)}$$

Nodal Analysis

- Assign a reference node
- Use KCL at each subsequent node where the voltage is unknown
- Form and solve equations for **voltages**

Nodal Analysis Example (I)

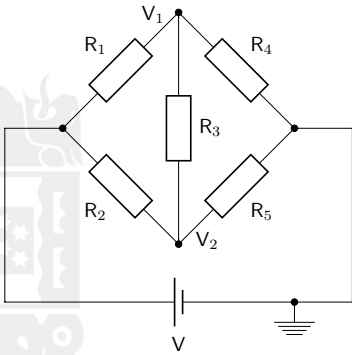


- KCL @ V_1

$$\frac{V - v_1}{R_1} + \frac{v_2 - v_1}{R_3} + \frac{-v_1}{R_4} = 0$$
- KCL @ V_2 :

$$\frac{V - v_2}{R_2} + \frac{v_1 - v_2}{R_3} + \frac{-v_2}{R_5} = 0$$

Mesh Analysis Example (II)
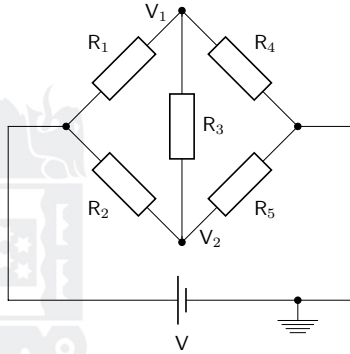
$$R_1 = R_5 = 2\Omega, R_2 = R_4 = 4\Omega, R_3 = 3\Omega, V = 5V$$



$$\frac{5 - v_1}{2} + \frac{v_2 - v_1}{3} + \frac{-v_1}{4} = 0$$

$$\frac{5 - v_2}{4} + \frac{v_1 - v_2}{3} + \frac{-v_2}{2} = 0$$

$$\begin{bmatrix} -\frac{1}{2} + \frac{-1}{3} + \frac{-1}{4} & \frac{1}{3} \\ \frac{-1}{2} + \frac{1}{3} + \frac{-1}{4} & -\frac{5}{4} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -\frac{5}{4} \\ -\frac{5}{4} \end{bmatrix}$$

Nodal Analysis Example (III)

$$\begin{bmatrix} -13 & 4 \\ 4 & -13 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -30 \\ -15 \end{bmatrix}$$

- 2 Eqns. in 2 unknowns
- Solve by substitution, computer, or Cramer's Rule

Solving matrix equations

- In Mesh / Nodal Analysis, often have to solve $Ax = b$, where
 - A is an $n \times n$ matrix of coefficients
 - x is a vector of unknown variables, e.g., i_1, \dots, i_3 or v_1, v_2
 - b is a vector of known voltages or currents

Matrix Equations

$$\begin{bmatrix} -13 & 4 \\ 4 & -13 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -30 \\ -15 \end{bmatrix}$$

$$\begin{bmatrix} -8 & 3 & 5 \\ 3 & -12 & 4 \\ 5 & 4 & -12 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -5 \\ 0 \\ 0 \end{bmatrix}$$

$$Ax = b$$

Cramer's Rule Example

- Cramer's Rule says we can find x_i by replacing the i th column of A with b and calculating the normalised determinant of the resulting matrix, A_i :

$$A : \begin{bmatrix} -8 & 3 & 5 \\ 3 & -12 & 4 \\ 5 & 4 & -12 \end{bmatrix}$$

$$\Rightarrow A_1 : \begin{bmatrix} -5 & 3 & 5 \\ 0 & -12 & 4 \\ 0 & 4 & -12 \end{bmatrix}$$

$$\Rightarrow A_2 : \begin{bmatrix} -8 & -5 & 5 \\ 3 & 0 & 4 \\ 5 & 0 & -12 \end{bmatrix}$$

$$\Rightarrow A_3 : \begin{bmatrix} -8 & 3 & -5 \\ 3 & -12 & 0 \\ 5 & 4 & 0 \end{bmatrix}$$

Cramer's Rule

$$x_i = \frac{|A_i|}{|A|}$$

Example

- Find $|A|$, then find i_1, i_2, i_3

$$\begin{bmatrix} -8 & 3 & 5 \\ 3 & -12 & 4 \\ 5 & 4 & -12 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -5 \\ 0 \\ 0 \end{bmatrix}$$

Example

- Find $|A|$, then find v_1 and v_2

$$\begin{bmatrix} -13 & 4 \\ 4 & -13 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -30 \\ -15 \end{bmatrix}$$


Cramer's Rule

- Some (equivalent) conditions for valid results:
 - Need as many equations as unknowns
 - Need a unique solution for results to be valid
 - A must be square (i.e., $n \times n$)

Voltage Source


Voltage Source

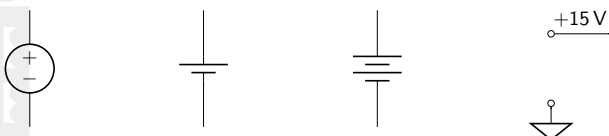- Ideally, maintains fixed voltage across its terminals *regardless of load*
- i.e., an ideal voltage source has 0 resistance
- e.g., behaves like an *ideal* battery




Current Source

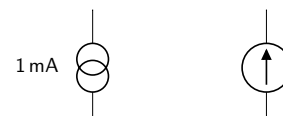- Ideally, provides a constant current *regardless of load*
- i.e. ideal current source has ∞ resistance.
- Practically – very complicated: Requires lots of semiconducting elements
- See more of this in ECEN303, ECEN403




Circuit Theorems

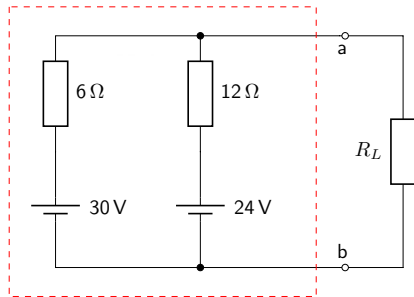- A common theme of this course is that complicated circuits can be reduced to much simpler ones.
- e.g., What does the circuit in the red box look like to the load, R_L ?




Thevenin's Theorem

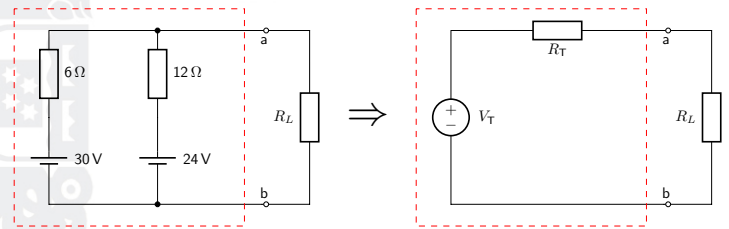- We can replace a two terminal network of resistors and energy sources with a *voltage* source V_T and a *series* resistance, R_T :
- V_T = open-cct voltage of the network
- $R_T = V_{OC}/I_{SC}$




Thevenin's Theorem Example

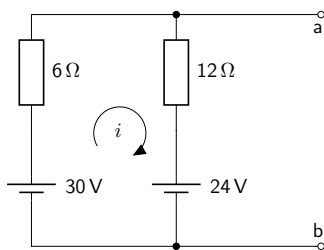- What is the Thevenin equivalent of this circuit?




Norton's Theorem

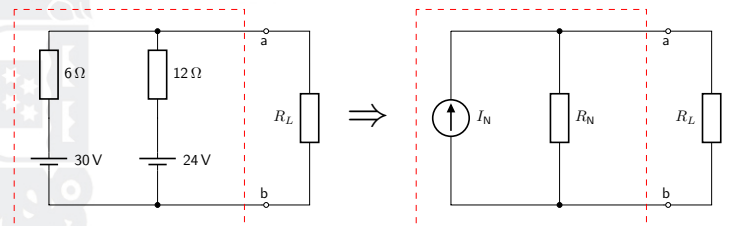- We can replace any two terminal network of resistors and energy sources with a *current* source and a *parallel* resistance, R_N :
- I_N = short-circuit current of the network
- $R_N = V_{OC}/I_{SC}$




Norton's Theorem Example

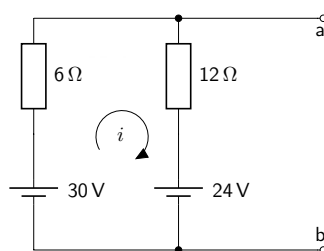- What is the Norton equivalent of this circuit?




Norton's Theorem Example (II)

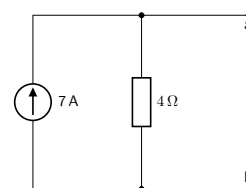- Example: What is the Norton equivalent of this circuit?
- Answer:



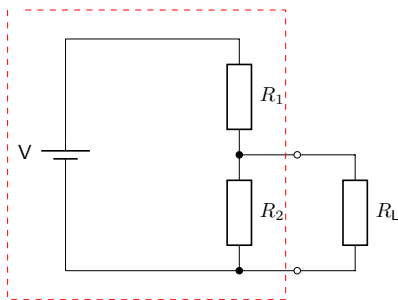Example: equivalent of voltage divider

- Find the Thevenin and Norton equivalents of a voltage divider
 - i.e. what is the equiv. cct inside the box?
 - Remove load
 - Find V_{OC}
 - Find I_{SC}




Source Resistance

- Another way to find R_T or R_N is to measure the resistance "looking into" the network, with sources zeroed, i.e.,:
 - Voltage sources shorted out ($V = 0$)
 - Current sources open-circuited ($I = 0$)

Source Resistance


- Remove load
- Short voltage source

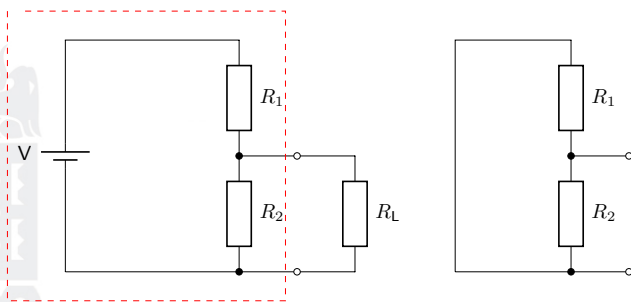

$$R_T = R_N = \frac{R_1 R_2}{R_1 + R_2}$$


Circuit Loading

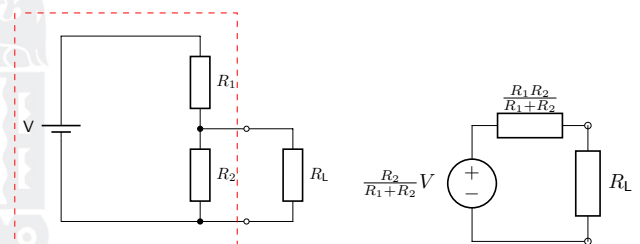- Previous example shows we can replace a voltage divider with a Thevenin equivalent V_T and series resistance, R_T .
- What happens when a load is connected?



Circuit Loading

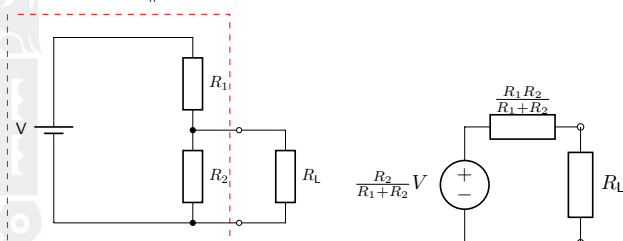- R_L & R_T form new voltage divider, so $V_L < V_T$
- Voltage drop, $V_L - V_T$ depends entirely on the ratio of R_L to $R_1 \parallel R_2$.
- If $R_L \ll R_1 \parallel R_2$, then $V_L \ll V_T$ 😞




Circuit Loading

- Practically, we can think of R_T as the **internal resistance** of the source
- We say R_L loads the source
- We can reduce loading by using smaller R_1, R_2 (stiff voltage divider – will see this in ECEN204)
- But: this leads to larger currents and more resistive heating


Circuit Loading Example

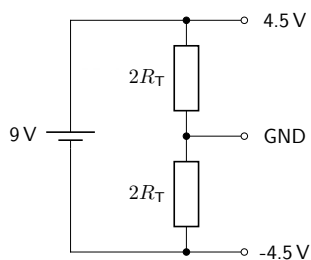- Design a power supply based on a 9V battery for an audio amplifier
- How big should R_T be?




Another example

- Find the Thevenin equivalent circuit

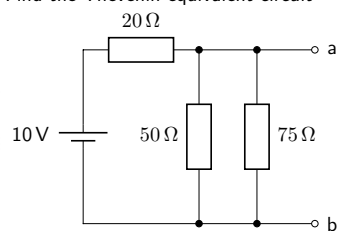

- $R_L = 100\Omega$ is connected between a & b.
- What is V_L ?
- What is P_L (power dissipated across R_L)?


Superposition

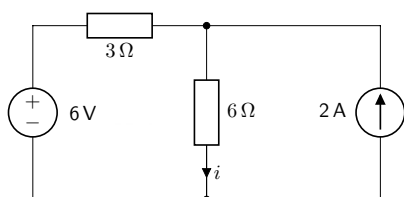


- Previously, had to use KCL + KVL around two loops to find i
- Alternatively, can consider effect of sources independently:

Superposition (II)

- Open-circuit the I source, find i_1 :

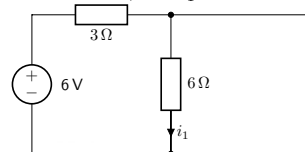



- Short-circuit V source, find i_2 :

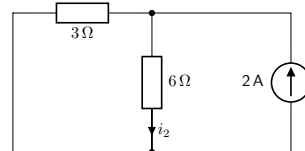


- By superposition, $i = i_1 + i_2$

(Aside:)Current Divider

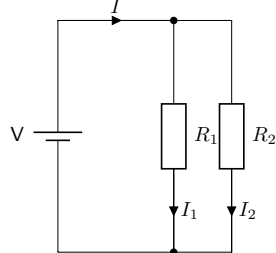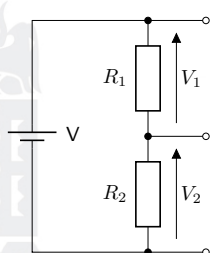- Consider the similarities between these two circuits:




Current Divider (II)

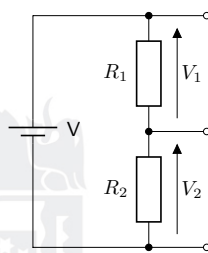

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$V = V_1 + V_2$$

$$V_1 = V \frac{R_1}{R_1 + R_2}$$

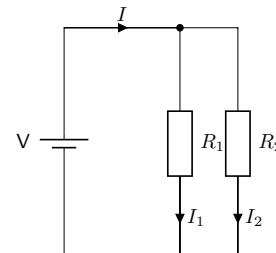

$$\frac{I_1}{I_2} = \frac{G_1}{G_2} = \frac{R_2}{R_1}$$

$$I = I_1 + I_2$$

$$I_1 = I \frac{G_1}{G_1 + G_2} = I \frac{R_2}{R_1 + R_2}$$

Summary



- Kirchhoff's Laws
- Mesh Analysis
- Nodal Analysis
- Cramer's Rule
- Circuit Theorems: $R_R = V_{OC}/I_{SC}$
- V & I Sources
- Superposition