

ECEN 405
Lab 1 PWM Submission

Daniel Eisen : 300447549

July 18, 2021

Deliverables

1. Capacitance:

$$C_1 = \frac{10k}{4 \cdot 8.2k \cdot 1k \cdot 30kHz}$$
$$= 1.016 \times 10^{-8}$$
$$C_1 = 10.16nF$$


2. Frequencies:

$$R_1 = 8.2k, R_2 = 10k, R_5 = 1k, C_1 = 10.16nF$$

$$F_t = \frac{(R_2 + R_3)}{4R_1(R_4 + R_5)C_1}$$
$$F_t\{R_3 = 1M, R_4 = 0\} = 3.03MHz$$
$$F_t\{R_3 = 0, R_4 = 100k\} = 297.1Hz$$

to match lab value : $F_t\{R_3 = 0, R_4 = 1M\} = 29.97Hz$

3. Schematic:

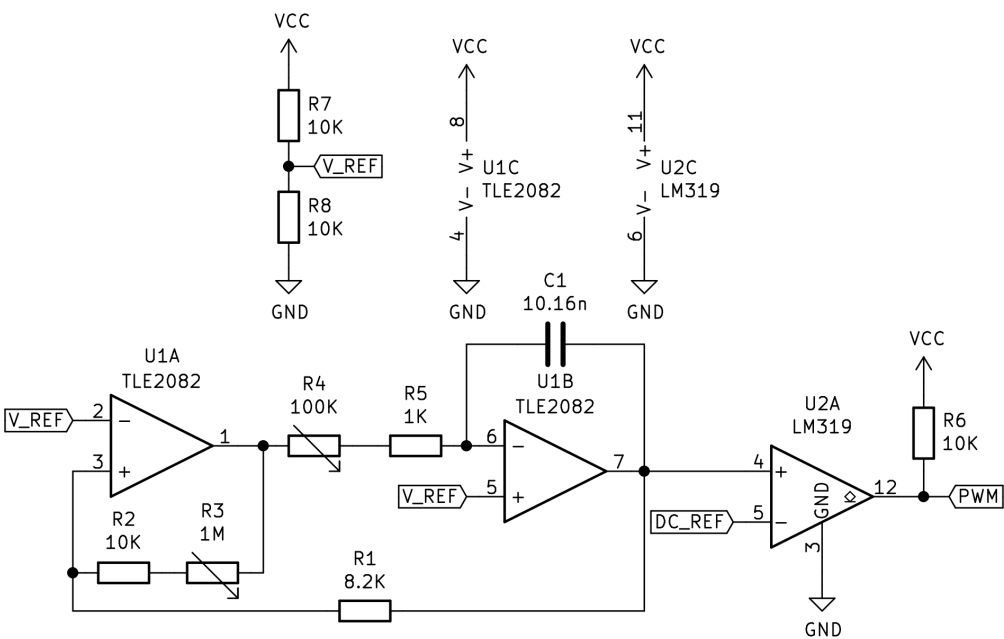

4. IRFBC40APBF: $R_{DS(on)} = 1.2$, $t_{c,on} = 13$, $t_{c,off} = 31$

$$\text{Conduction losses} = P_{cond} = R_{DS(on)} dI^2$$
$$= 1.2 \cdot 0.5 \cdot 1$$
$$= 0.6W$$


$$\text{Switching losses} = P_{sw} = \frac{1}{2} V_{in} I_o$$
$$@29.97Hz = 7.91\mu W$$
$$@297.1Hz = 78.4\mu W$$
$$@3.03MHz = 0.799W$$

5. Build it:




Danny B's approval of breadboarded circuit

6. Test it:

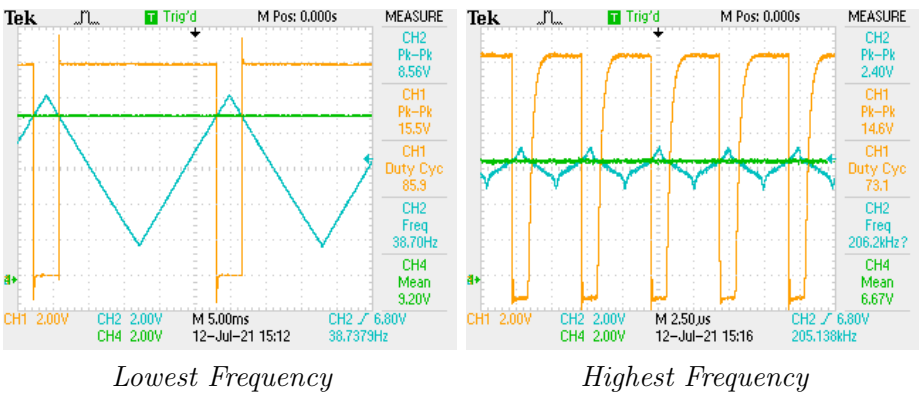

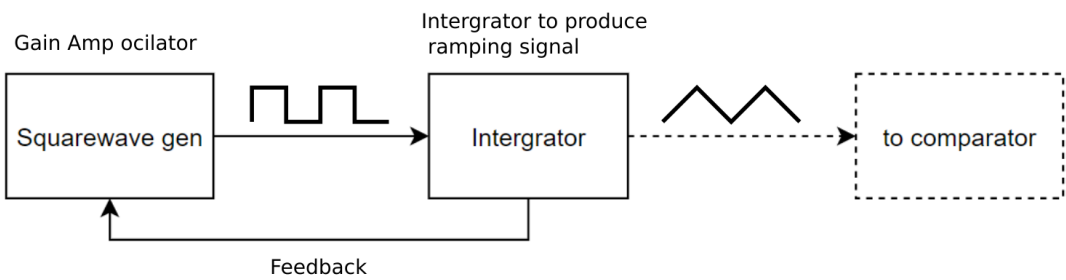7. This circuit is constructed in the real world on a breadboard. So it differs from ideal with parasitic capacitance, imperfect slew rates from the op-amps and comparators and possibly other non-ideal factors. Due to this the upper theoretical frequency (3Mhz) was could not be achieved, with only a recorded max of 200kHz.
8. The LM319 is a duel comparator chip, so to add an inverted output to the circuit the input just need to be switched and fed into the second comparator pins and its out also pulled up.
9. This circuit consists of two main subcircuits, and produces a triangle wave on its output to be fed to a comparator to produce the PWM signal.

The gain amp is unsatable with positive feedback and thus oscillates from rail to rail (R3 controls gain, ie scales f/a). An integrator then produces the output triangle wave. With R4 controlling the charge current for its feedback capacitor, thus controlling frequency.



Sub-circuits: Gain Amp Oscillator and Integrator: