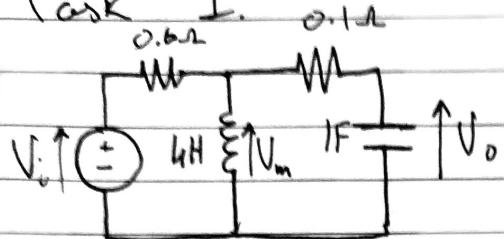


315 Clas 1

Examen:

Task 1.




$$V_i = V_m = 0.6 I_i$$





$$I_m = I_i - I_o$$

$$V_m = L_s I_m, \quad V_m - V_o = 0.1 I_o$$

$$V_o = \frac{1}{5} I_o$$

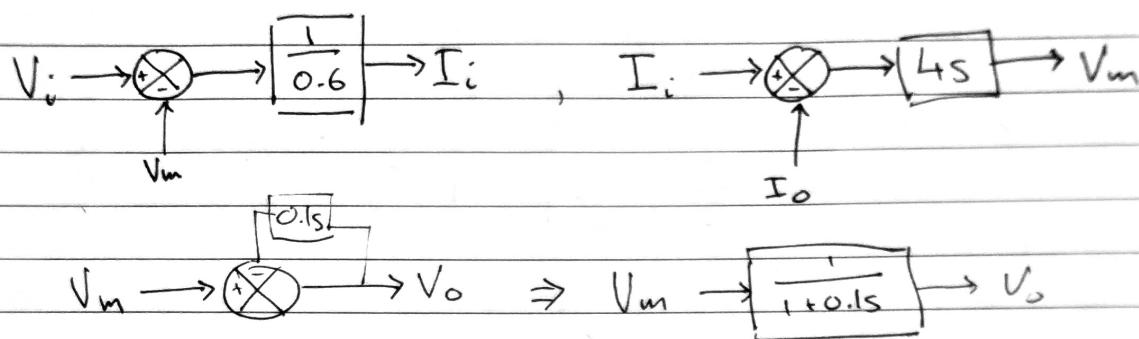

Combine:

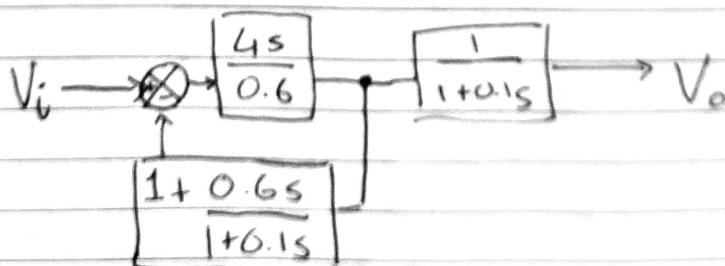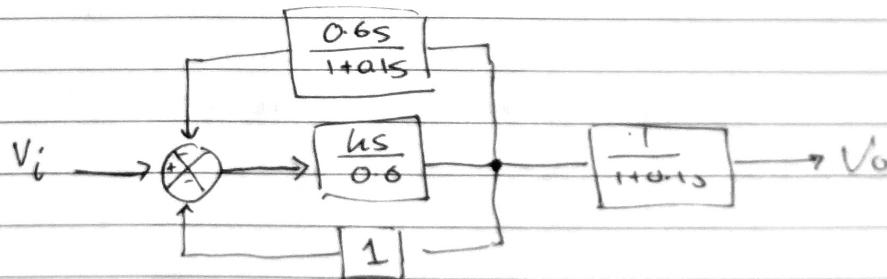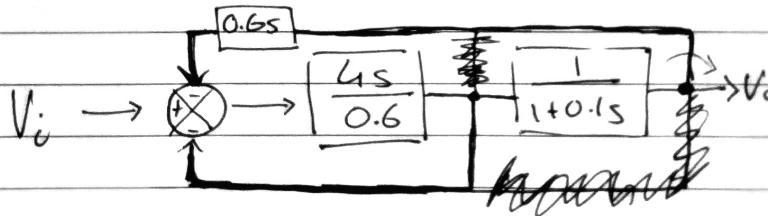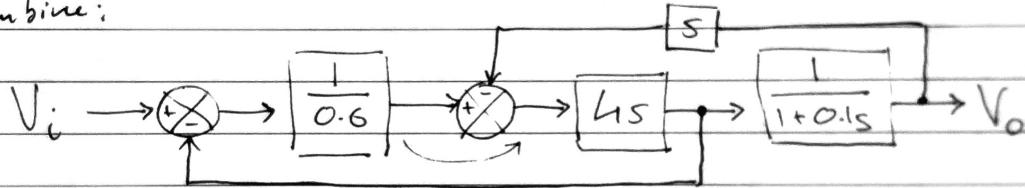

$$\frac{forward}{1 - loop} \Rightarrow \frac{L_S}{0.6} = \frac{L_S}{1 + (1 + \frac{0.6S}{1+0.1S} \cdot \frac{L_S}{0.6})}$$

$$= \frac{L_S}{0.6 \left(1 + \frac{L_S}{0.6} + \frac{L_S^2}{1.01S} \right)} = \frac{L_S}{0.6 (2.85^2 + 4.06S + 0.6)}$$

$$\Rightarrow V_o \rightarrow \boxed{\frac{L_S (1 + 0.1S)}{2.85^2 + 4.06S + 0.6}} \rightarrow \boxed{\frac{1}{1 + 0.1S}} \rightarrow V_o$$

$\therefore \frac{V_o}{V_i} = \frac{L_S}{2.85^2 + 4.06S + 0.6}$

$$(step input) \quad V_o(t) = \mathcal{I}^{-1} \left\{ \frac{1}{s} \cdot \frac{L_S}{2.85^2 + 4.06S + 0.6} \right\}$$

$$\Rightarrow \frac{L_S}{2.8} \cdot \left[\frac{1}{s^2 + 1.45s + 0.2143} \right]$$

$$\text{Via quadratic eq.} \Rightarrow \frac{1}{(s+0.167)(s+1.283)} = \frac{A}{s+0.167} + \frac{B}{s+1.283}$$



$$1 = A(s+1.283) + B(s+0.167)$$

$$A = 0.896 \quad B = -0.896$$

$$\therefore \frac{L_S}{2.8} \mathcal{I}^{-1} \left\{ \frac{0.896}{s+0.167} - \frac{0.896}{s+1.283} \right\}$$

$$= \frac{L_S}{2.8} \left[0.896 e^{-0.167t} - 0.896 e^{-1.283t} \right]$$

$$V_o(t) = 1.28 \left(e^{-0.167t} - e^{-1.283t} \right)$$

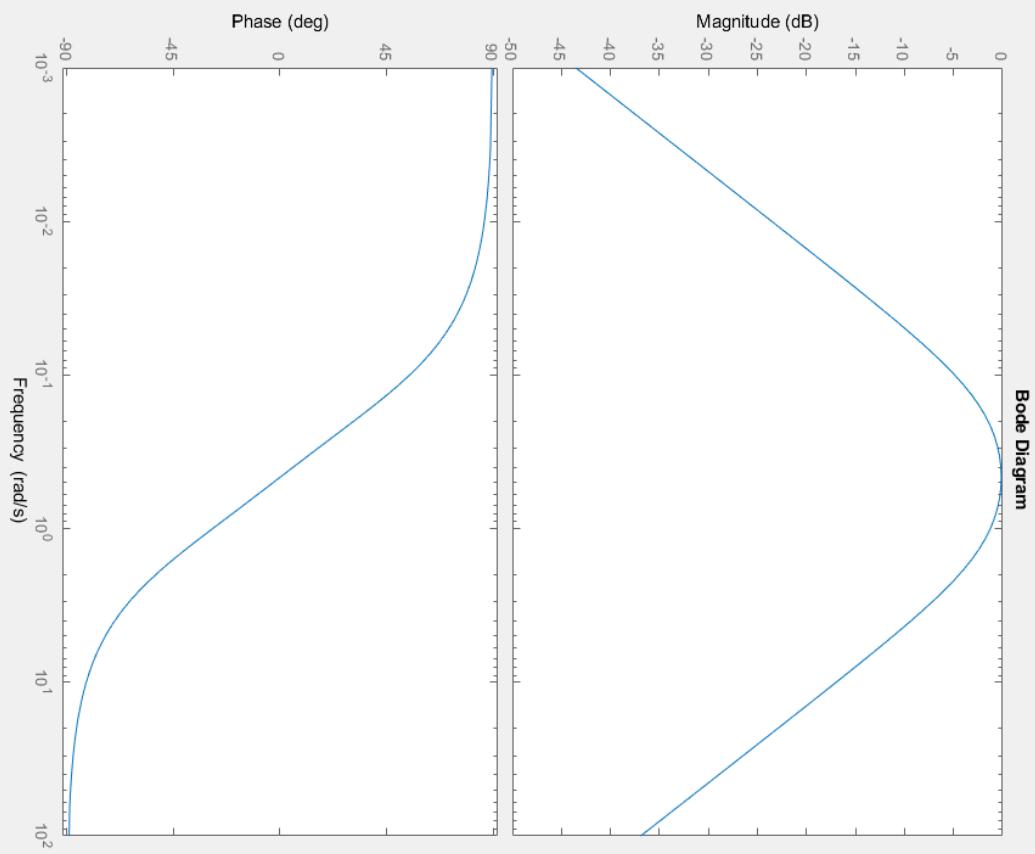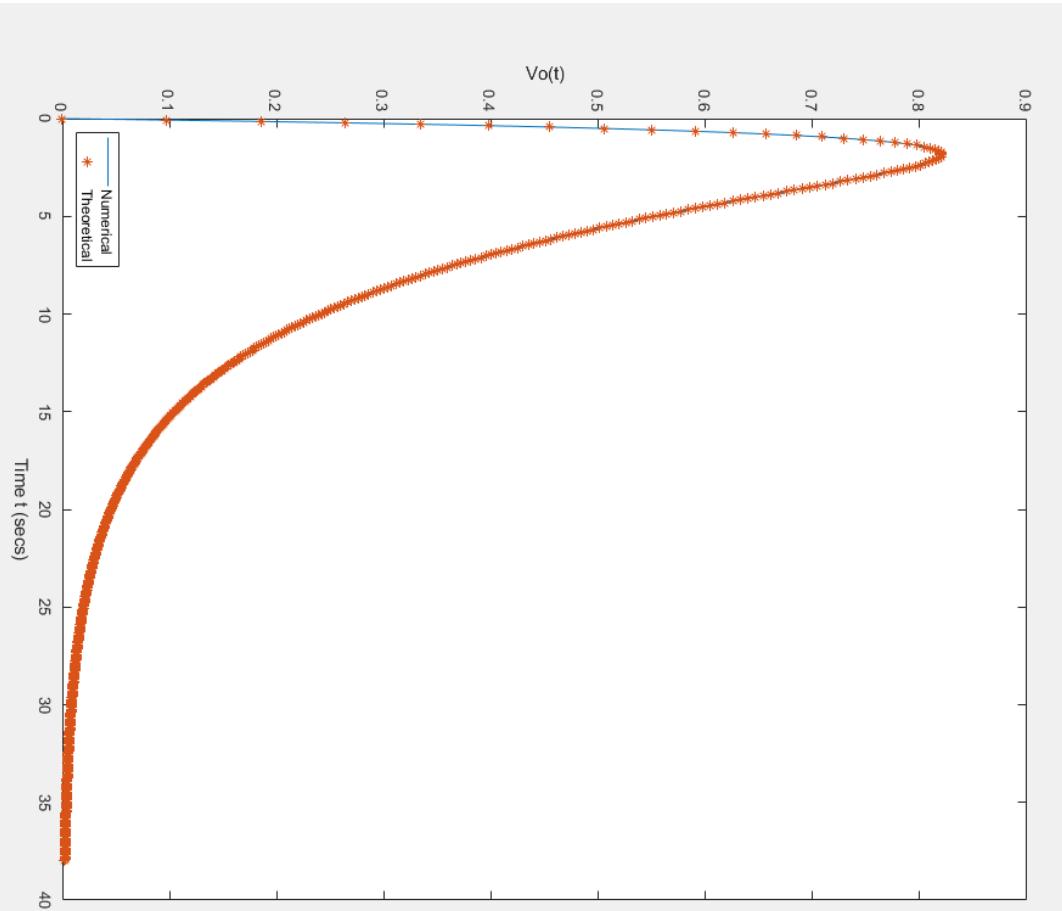

Task 2

Model: $T_1 \rightarrow T$

input

output

Assumptions: $T_0 = 25^\circ\text{C}$

$m = 10\text{ kg}, 10,000\text{ g}$

$A \approx \text{cyl/inner} = 2\pi r h + 2\pi r^2$

$\approx 2\pi(0.15)(0.2) + 2\pi(0.15)^2$

$A = 0.32\text{ m}^2$

$A \approx \frac{1}{3}\text{ m}^2$

Given: $C = 0.45 \text{ J/g}\cdot\text{K}$ $h = 100 \text{ W/m}^2\text{k}$

$q' = hA(T_1 - T)$


$q' \propto \Delta T$

$q' = C \Delta T$






$\therefore q' = m C \Delta T \Rightarrow q' = m \left(\frac{d}{dt} T \right)$

$$Q = hA(T_1 - T)$$

$$Q_3 = mC[sT - T_0]$$

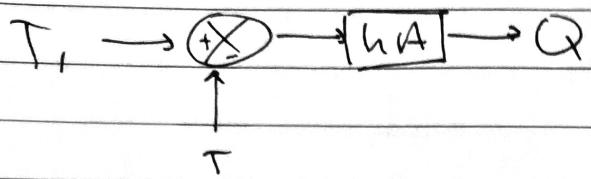
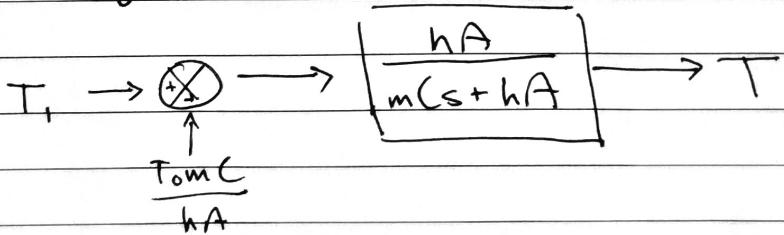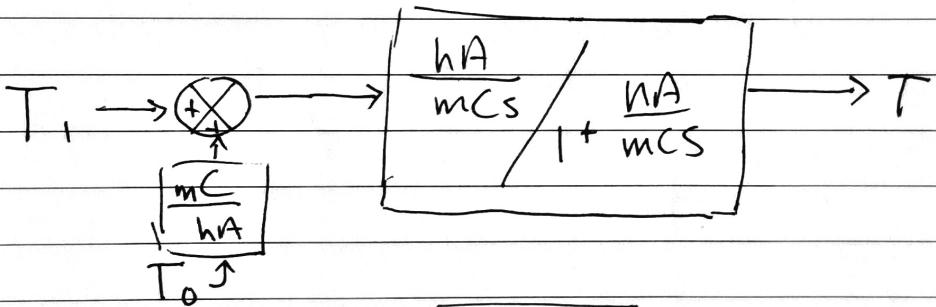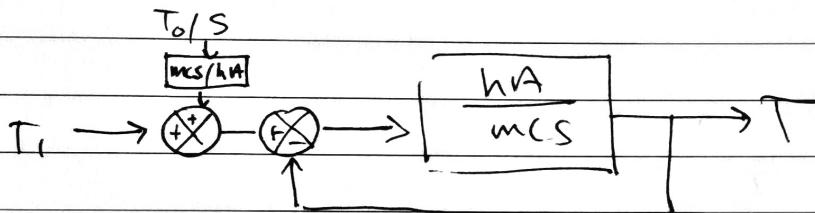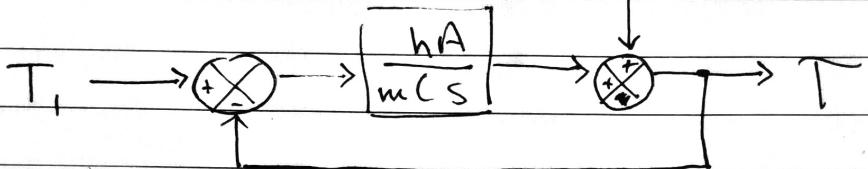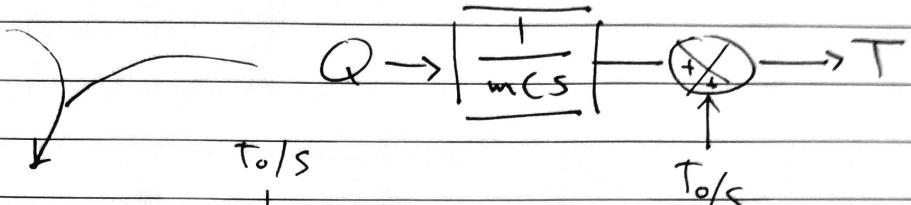
$$\therefore T = \frac{Q}{mCs} + \frac{T_0}{s}$$




time response of initial conditions

$$f^{-1} \left\{ \frac{T_{0mc}}{mCs + hA} \right\} \Rightarrow T_0 e^{-\frac{hAt}{mC}}$$

See plots - eCode

Time estimate ~~approx 60-70 seconds to reach 80°C~~

~ 51 secs

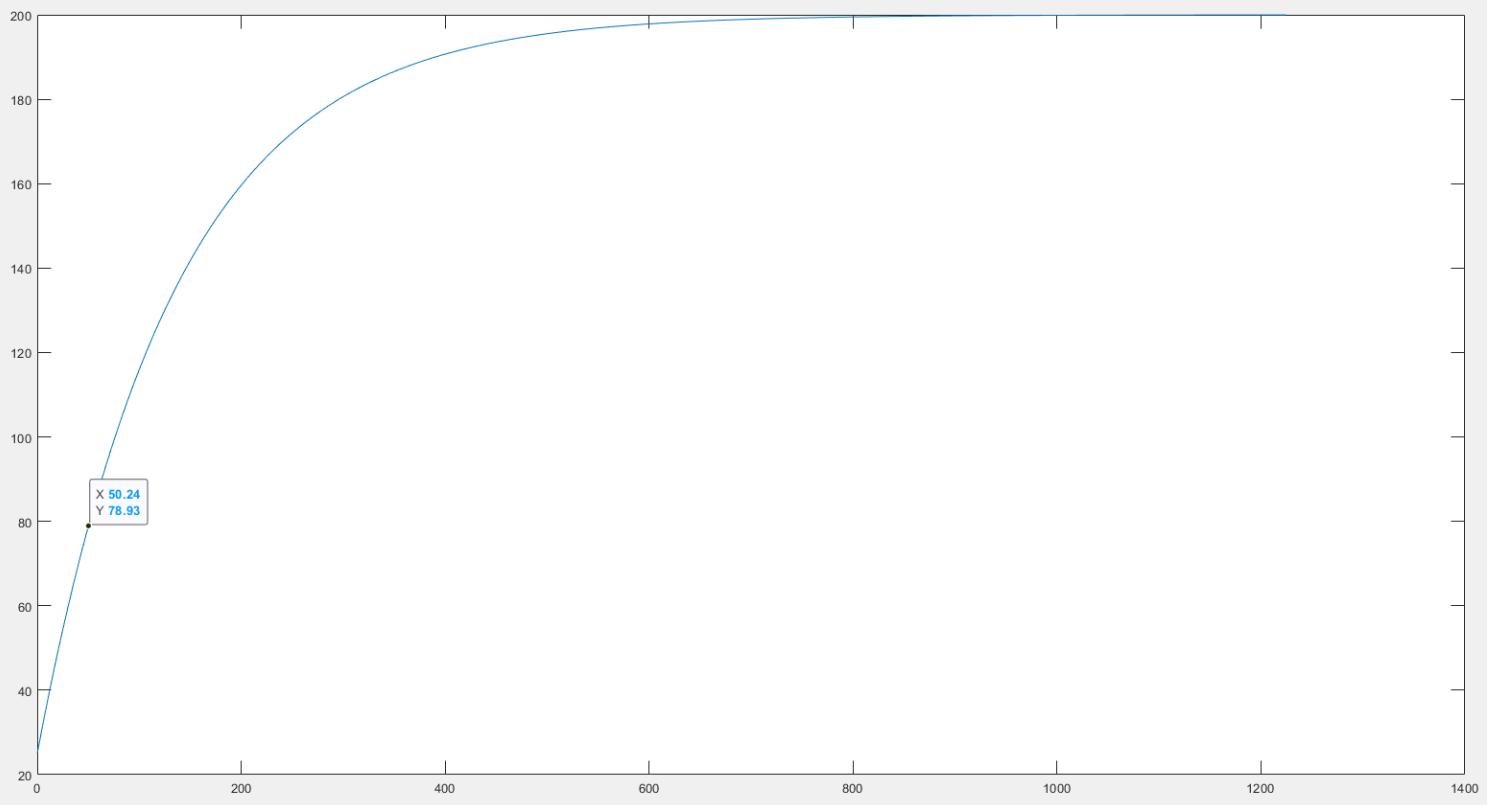

```
clear;

s = tf('s');

T0 = 25;
T1 = 200;
m=10000;
A=0.33;

C=0.45;
h=100;

sys = (h*A) / (m*C*s + h*A);

opt = stepDataOptions('StepAmplitude', T1);

figure(2);
[x,t] = step(sys,opt);

init = T0*exp((-h*A*t)/(m*C));

plot(t,x+init)
```