

**Section 2.4 Kirchoff's Laws:**


- 2.18** a) Find the currents  $i_1$  and  $i_2$  in the circuit in Fig. P2.18.

PSPICE

MULTISIM

- b) Find the voltage  $v_o$ .

- c) Verify that the total power developed equals the total power dissipated.

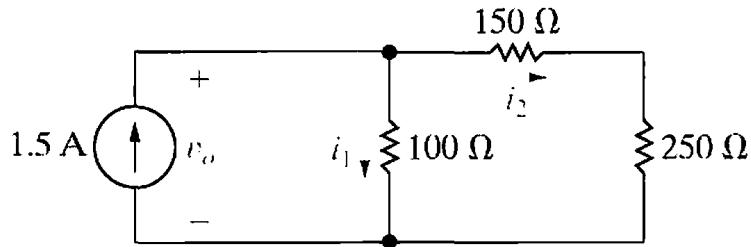
**Figure P2.18**

- 2.19** Given the circuit shown in Fig. P2.19, find

PSPICE

MULTISIM

- a) the value of  $i_a$ ,  
 b) the value of  $i_b$ ,  
 c) the value of  $v_o$ ,  
 d) the power dissipated in each resistor,  
 e) the power delivered by the 50 V source.

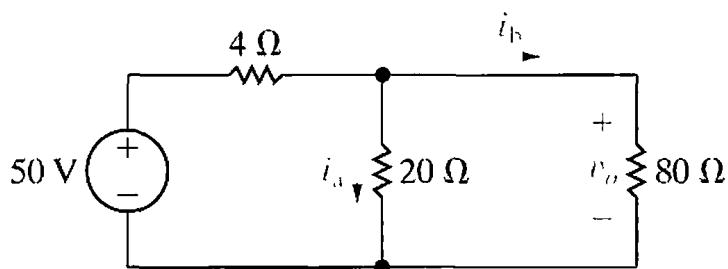
**Figure P2.19**

- 2.20** The current  $i_a$  in the circuit shown in Fig. P2.20 is 2 mA. Find (a)  $i_o$ ; (b)  $i_g$ ; and (c) the power delivered by the independent current source.

PSPICE


MULTISIM

Figure P2.20

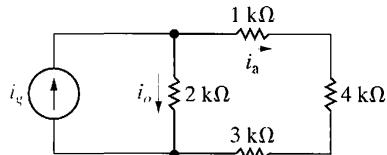


- 2.21** The current  $i_o$  in the circuit in Fig. P2.21 is 1 A.
- MULTISIM
- Find  $i_1$ .
  - Find the power dissipated in each resistor.
  - Verify that the total power dissipated in the circuit equals the power developed by the 150 V source.

Figure P2.21

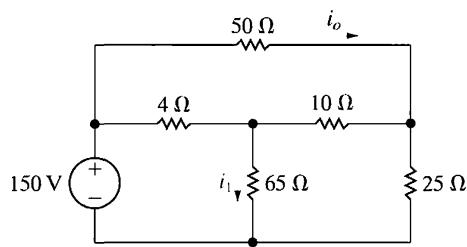


- 2.22** The voltage across the 16 Ω resistor in the circuit in Fig. P2.22 is 80 V, positive at the upper terminal.
- MULTISIM
- Find the power dissipated in each resistor.
  - Find the power supplied by the 125 V ideal voltage source.
  - Verify that the power supplied equals the total power dissipated.

Figure P2.22

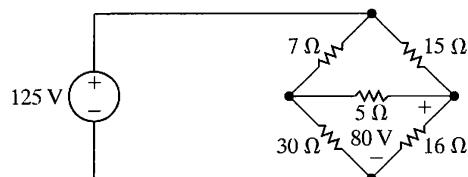


- 2.23** For the circuit shown in Fig. P2.23, find (a)  $R$  and (b) the power supplied by the 240 V source.
- MULTISIM

Figure P2.23

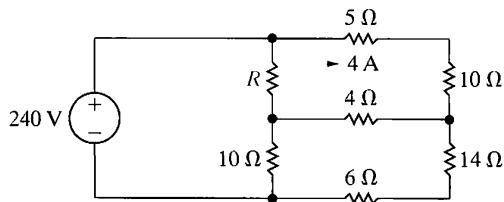


- 2.24** The variable resistor  $R$  in the circuit in Fig. P2.24 is adjusted until  $v_a$  equals 60 V. Find the value of  $R$ .
- MULTISIM

Figure P2.24

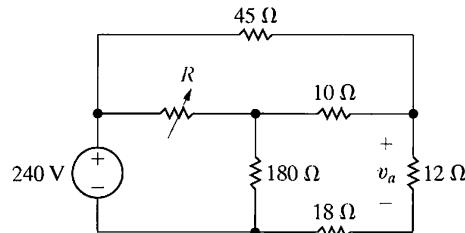


- 2.25** The currents  $i_1$  and  $i_2$  in the circuit in Fig. P2.25 are 21 A and 14 A, respectively.
- Find the power supplied by each voltage source.
  - Show that the total power supplied equals the total power dissipated in the resistors.

Figure P2.25

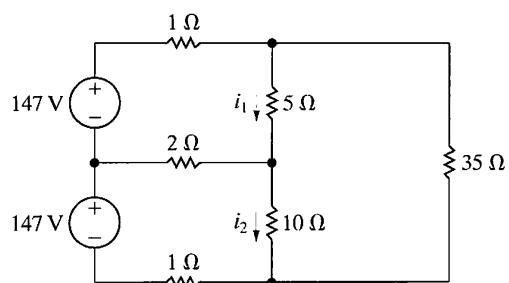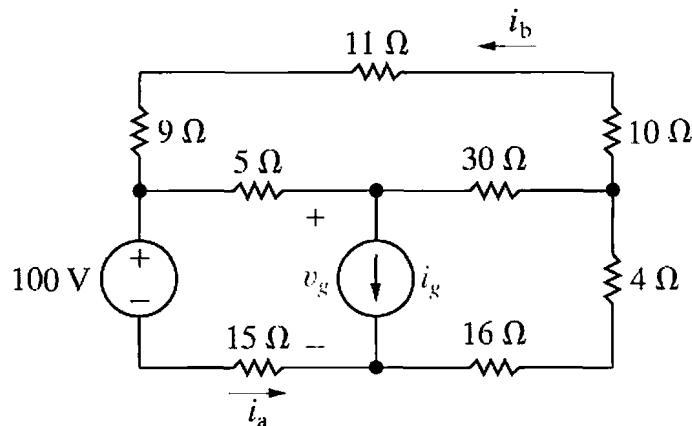


- 2.26** The currents  $i_a$  and  $i_b$  in the circuit in Fig. P2.26 are 4 A and -2 A, respectively.
- MULTISIM
- Find  $i_g$ .
  - Find the power dissipated in each resistor.


- c) Find  $v_g$ .
- d) Show that the power delivered by the current source is equal to the power absorbed by all the other elements.

**Figure P2.26****Section 4.2 Nodal Analysis:**

- 4.6** Use the node-voltage method to find  $v_1$  and  $v_2$  in  
PSPICE MULTISIM the circuit in Fig. P4.6.

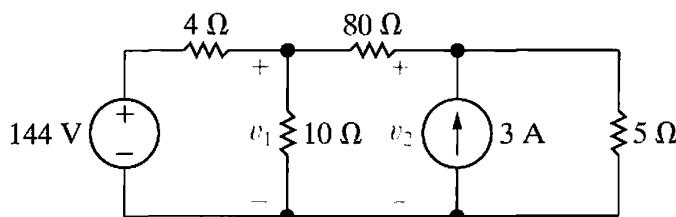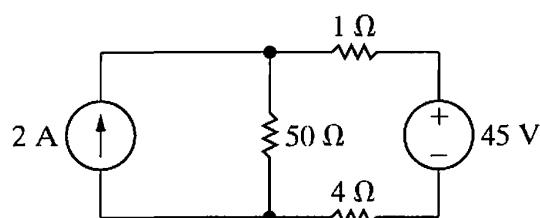**Figure P4.6**


- 4.7** Use the node-voltage method to find how much  
PSPICE MULTISIM power the 2 A source extracts from the circuit in  
Fig. P4.7.

**Figure P4.7**

- 4.8** Use the node-voltage method to find  $v_1$  and  $v_2$  in the circuit shown in Fig. P4.8.

PSPICE  
MULTISIM


Figure P4.8

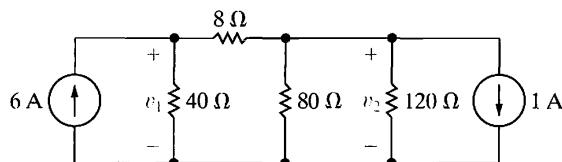

- 4.9** Use the node-voltage method to find  $v_o$  in the circuit in Fig. P4.9.

PSPICE  
MULTISIM

Figure P4.9

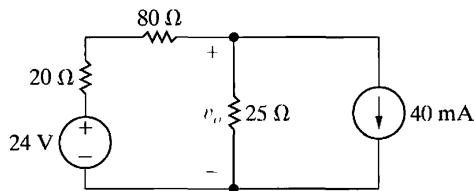

- 4.10** a) Find the power developed by the 40 mA current source in the circuit in Fig. P4.9.  
b) Find the power developed by the 24 V voltage source in the circuit in Fig. P4.9.  
c) Verify that the total power developed equals the total power dissipated.

- 4.11** A 50 Ω resistor is connected in series with the 40 mA current source in the circuit in Fig. P4.9.

PSPICE  
MULTISIM

- a) Find  $v_o$ .  
b) Find the power developed by the 40 mA current source.  
c) Find the power developed by the 24 V voltage source.  
d) Verify that the total power developed equals the total power dissipated.  
e) What effect will any finite resistance connected in series with the 40 mA current source have on the value of  $v_o$ ?


- 4.12** The circuit shown in Fig. P4.12 is a dc model of a residential power distribution circuit.

PSPICE  
MULTISIM

- a) Use the node-voltage method to find the branch currents  $i_1 - i_6$ .

- b) Test your solution for the branch currents by showing that the total power dissipated equals the total power developed.


Figure P4.12

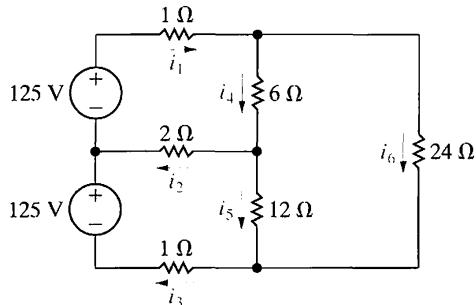

- 4.13** a) Use the node-voltage method to find the branch currents  $i_a - i_e$  in the circuit shown in Fig. P4.13.


- b) Find the total power developed in the circuit.

Figure P4.13

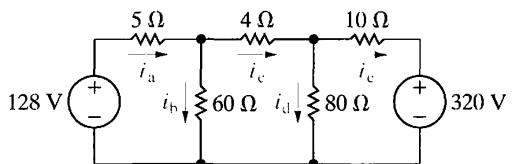


- 4.14** Use the node-voltage method to find the total power dissipated in the circuit in Fig. P4.14.


Figure P4.14

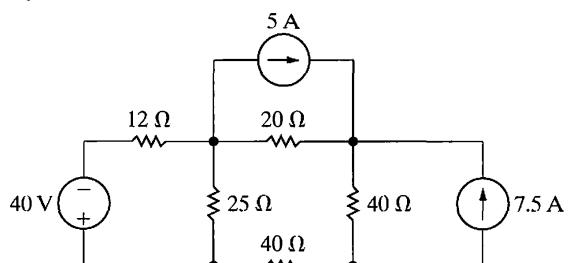

- PSPICE  
MULTISIM
- 4.15** a) Use the node-voltage method to find  $v_1$ ,  $v_2$ , and  $v_3$  in the circuit in Fig. P4.15.
- b) How much power does the 40 V voltage source deliver to the circuit?

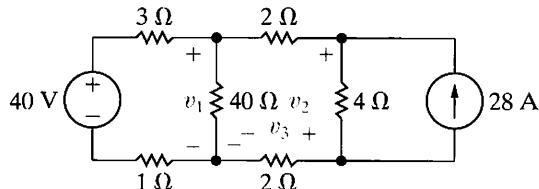
**Figure P4.15**

- PSPICE  
MULTISIM
- 4.16** a) Use the node-voltage method to show that the output voltage  $v_o$  in the circuit in Fig. P4.16 is equal to the average value of the source voltages.
- b) Find  $v_o$  if  $v_1 = 100 \text{ V}$ ,  $v_2 = 80 \text{ V}$ , and  $v_3 = -60 \text{ V}$ .

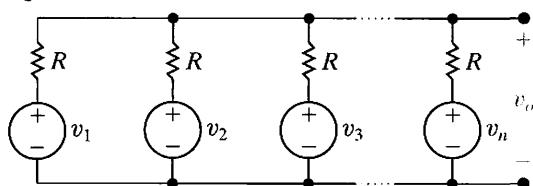
**Figure P4.16**

#### Section 4.4


- PSPICE  
MULTISIM
- 4.21** Use the node-voltage method to find  $i_o$  in the circuit in Fig. P4.21.

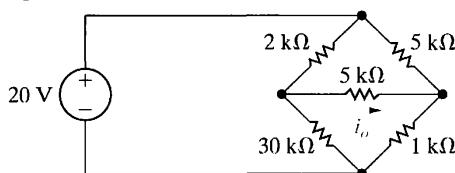**Figure P4.21**


- PSPICE  
MULTISIM
- 4.22** a) Use the node-voltage method to find the branch currents  $i_1$ ,  $i_2$ , and  $i_3$  in the circuit in Fig. P4.22.
- b) Check your solution for  $i_1$ ,  $i_2$ , and  $i_3$  by showing that the power dissipated in the circuit equals the power developed.

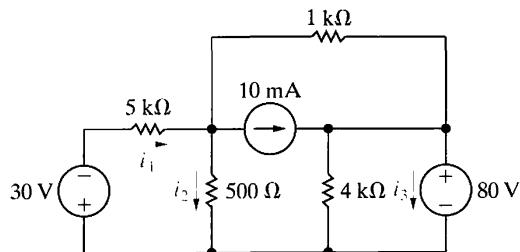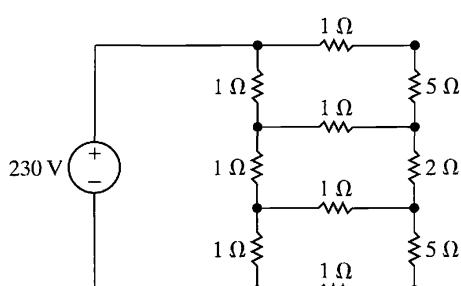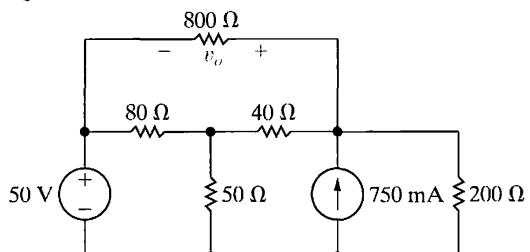**Figure P4.22**

- 4.23** a) Use the node-voltage method to find the power dissipated in the 2 Ω resistor in the circuit in Fig. P4.23.
- b) Find the power supplied by the 230 V source.


**Figure P4.23**

- PSPICE  
MULTISIM
- 4.24** Use the node-voltage method to find the value of  $v_o$  in the circuit in Fig. P4.24.


**Figure P4.24**

### Section 4.5 Mesh Analysis:

- 4.31** Solve Problem 4.12 using the mesh-current method.
- 4.32** Solve Problem 4.13 using the mesh-current method.
- 4.33** a) Use the mesh-current method to find the branch currents  $i_a$ ,  $i_b$ , and  $i_c$  in the circuit in Fig. P4.33.  
PSPICE MULTISIM
- b) Repeat (a) if the polarity of the 60 V source is reversed.

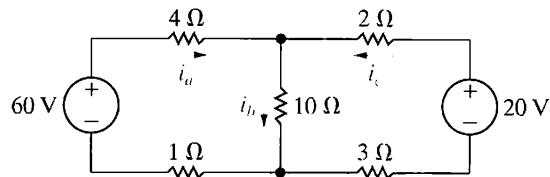**Figure P4.33**

- 4.34** a) Use the mesh-current method to find the total power developed in the circuit in Fig. P4.34.  
PSPICE MULTISIM
- b) Check your answer by showing that the total power developed equals the total power dissipated.

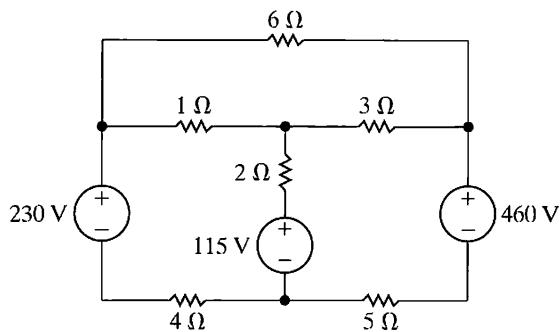
**Figure P4.34**

- 4.35** Solve Problem 4.21 using the mesh-current method.
- 4.36** Solve Problem 4.23 using the mesh-current method.

### Section 4.9 Thevenin and Norton Equivalents


- PSPICE  
MULTISIM
- 4.59** a) Use a series of source transformations to find the current  $i_o$  in the circuit in Fig. P4.59.  
 b) Verify your solution by using the node-voltage method to find  $i_o$ .

Figure P4.59

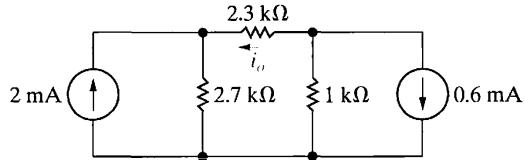


- PSPICE  
MULTISIM
- 4.60** a) Use a series of source transformations to find  $i_o$  in the circuit in Fig. P4.60.  
 b) Verify your solution by using the mesh-current method to find  $i_o$ .

Figure P4.60

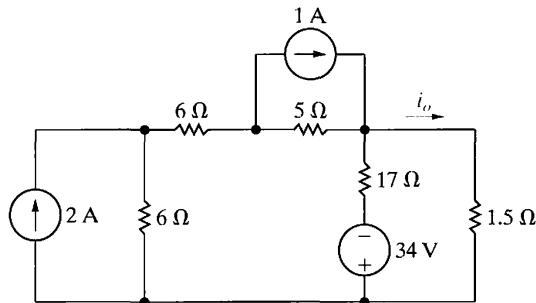


- PSPICE  
MULTISIM
- 4.61** a) Find the current in the  $10 \text{ k}\Omega$  resistor in the circuit in Fig. P4.61 by making a succession of appropriate source transformations.  
 b) Using the result obtained in (a), work back through the circuit to find the power developed by the  $100 \text{ V}$  source.

Figure P4.61

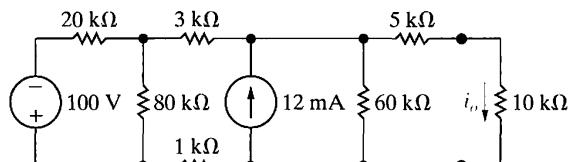

- PSPICE  
MULTISIM
- 4.62** a) Use source transformations to find  $v_o$  in the circuit in Fig. P4.62.  
 b) Find the power developed by the  $520 \text{ V}$  source.  
 c) Find the power developed by the  $1 \text{ A}$  current source.  
 d) Verify that the total power developed equals the total power dissipated.


Figure P4.62

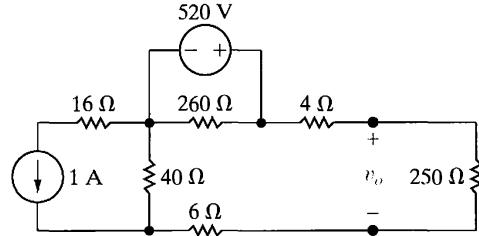

### Section 4.10 Thevenin and Norton Equivalents


- PSPICE  
MULTISIM
- 4.63** Find the Thévenin equivalent with respect to the terminals a,b for the circuit in Fig. P4.63.

Figure P4.63

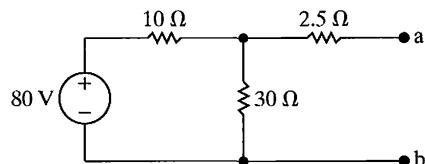


- PSPICE  
MULTISIM
- 4.64** Find the Norton equivalent with respect to the terminals a,b in the circuit in Fig. P4.64.


Figure P4.64

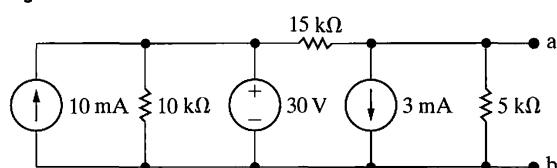


- PSPICE  
MULTISIM
- 4.65** a) Find the Thévenin equivalent with respect to the terminals a,b for the circuit in Fig. P4.65 by finding the open-circuit voltage and the short-circuit current.  
 b) Solve for the Thévenin resistance by removing the independent sources. Compare your result to the Thévenin resistance found in (a).

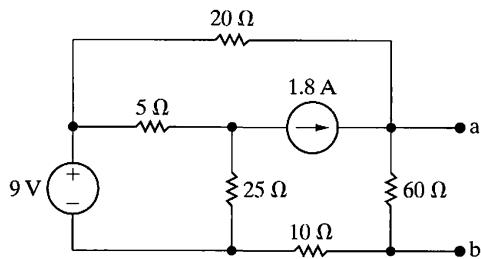**Figure P4.65**


- 4.66** Find the Thévenin equivalent with respect to the terminals a,b for the circuit in Fig. P4.66.

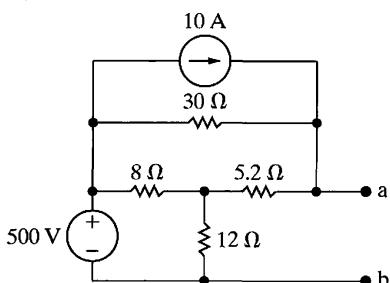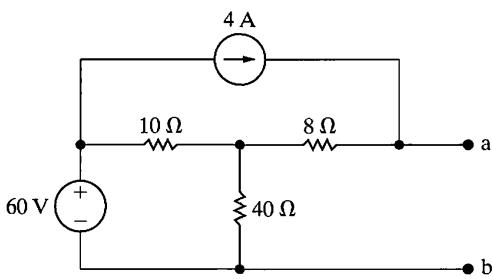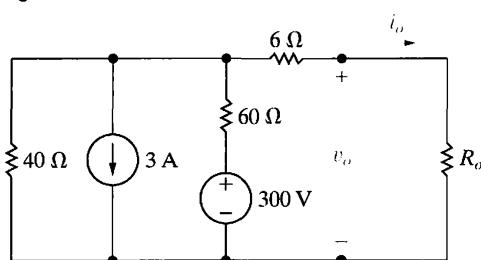**Figure P4.66**

- 4.67** Find the Norton equivalent with respect to the terminals a,b for the circuit in Fig. P4.67.

**Figure P4.67**

- 4.68** Determine  $i_o$  and  $v_o$  in the circuit shown in Fig. P4.68 when  $R_o$  is a resistor from Appendix H whose value is less than  $100\ \Omega$ .

**Figure P4.68**


- 4.69** An automobile battery, when connected to a car radio, provides 12.5 V to the radio. When connected to a set of headlights, it provides 11.7 V to the headlights. Assume the radio can be modeled as a  $6.25\ \Omega$  resistor and the headlights can be modeled as a  $0.65\ \Omega$  resistor. What are the Thévenin and Norton equivalents for the battery?

- 4.70** A Thévenin equivalent can also be determined from measurements made at the pair of terminals of interest. Assume the following measurements were made at the terminals a,b in the circuit in Fig. P4.70.

When a  $20\ \Omega$  resistor is connected to the terminals a,b, the voltage  $v_{ab}$  is measured and found to be 100 V.


When a  $50\ \Omega$  resistor is connected to the terminals a,b, the voltage is measured and found to be 200 V.

Find the Thévenin equivalent of the network with respect to the terminals a,b.

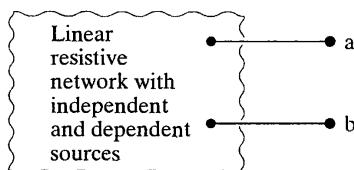**Figure P4.70**

- 4.71** A voltmeter with a resistance of  $85.5\ k\Omega$  is used to measure the voltage  $v_{ab}$  in the circuit in Fig. P4.71.


- What is the voltmeter reading?
- What is the percentage of error in the voltmeter reading if the percentage of error is defined as  $[(\text{measured} - \text{actual})/\text{actual}] \times 100\%$ ?

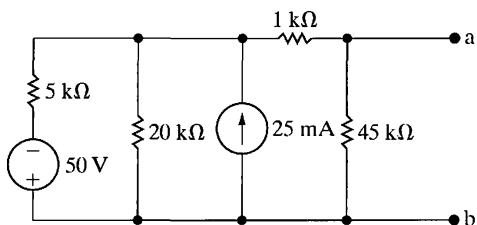**Figure P4.71**

**Section 4.13 Superposition**


- 4.91** a) Use the principle of superposition to find the voltage  $v$  in the circuit of Fig. P4.91.  
PSPICE  
MULTISIM
- b) Find the power dissipated in the  $10\ \Omega$  resistor.

Figure P4.91

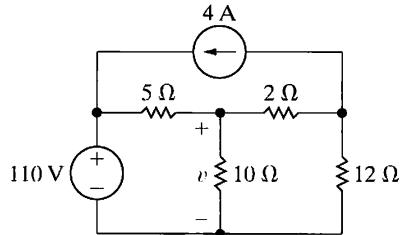


- 4.92** Use superposition to solve for  $i_o$  and  $v_o$  in the circuit in Fig. P4.92.

Figure P4.92

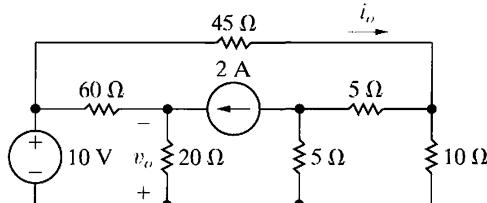


- 4.93** Use the principle of superposition to find the voltage  $v_o$  in the circuit in Fig. P4.93.  
PSPICE  
MULTISIM

Figure P4.93

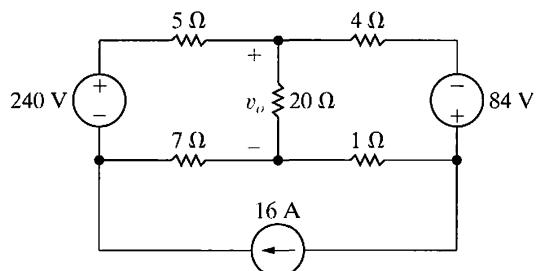


- 4.94** Use the principle of superposition to find the current  $i_o$  in the circuit shown in Fig. P4.94.  
PSPICE  
MULTISIM

Figure P4.94

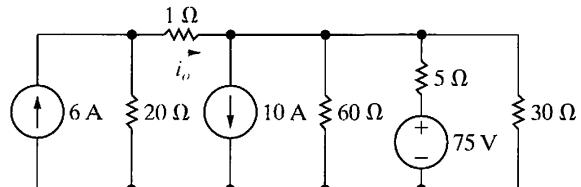


- 4.95** a) In the circuit in Fig. P4.95, before the  $5\text{ mA}$  current source is attached to the terminals a,b, the current  $i_o$  is calculated and found to be  $3.5\text{ mA}$ . Use superposition to find the value of  $i_o$  after the current source is attached.  
PSPICE  
MULTISIM
- b) Verify your solution by finding  $i_o$  when all three sources are acting simultaneously.

Figure P4.95

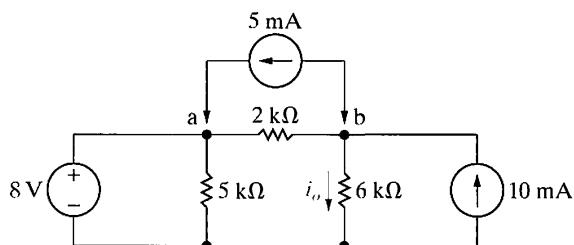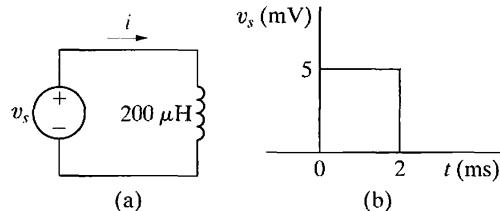


- 6.3** The voltage at the terminals of the  $200 \mu\text{H}$  inductor in Fig. P6.3(a) is shown in Fig. P6.3(b). The inductor current  $i$  is known to be zero for  $t \leq 0$ .

- a) Derive the expressions for  $i$  for  $t \geq 0$ .  
b) Sketch  $i$  versus  $t$  for  $0 \leq t \leq \infty$ .

**Figure P6.3**


- 6.4** The triangular current pulse shown in Fig. P6.4 is applied to a  $20 \text{ mH}$  inductor.

- a) Write the expressions that describe  $i(t)$  in the four intervals  $t < 0$ ,  $0 \leq t \leq 5 \text{ ms}$ ,  $5 \text{ ms} \leq t \leq 10 \text{ ms}$ , and  $t > 10 \text{ ms}$ .

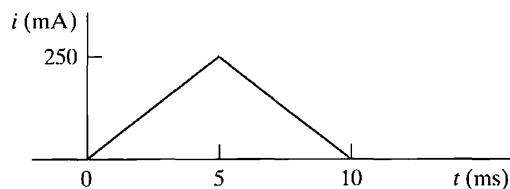**Figure P6.4**


- 6.5** The current in and the voltage across a  $5 \text{ H}$  inductor are known to be zero for  $t \leq 0$ . The voltage across the inductor is given by the graph in Fig. P6.5 for  $t \geq 0$ .

- a) Derive the expression for the current as a function of time in the intervals  $0 \leq t \leq 1 \text{ s}$ ,  $1 \text{ s} \leq t \leq 3 \text{ s}$ ,  $3 \text{ s} \leq t \leq 5 \text{ s}$ ,  $5 \text{ s} \leq t \leq 6 \text{ s}$ , and  $6 \text{ s} \leq t < \infty$ .  
b) For  $t > 0$ , what is the current in the inductor when the voltage is zero?  
c) Sketch  $i$  versus  $t$  for  $0 \leq t < \infty$ .

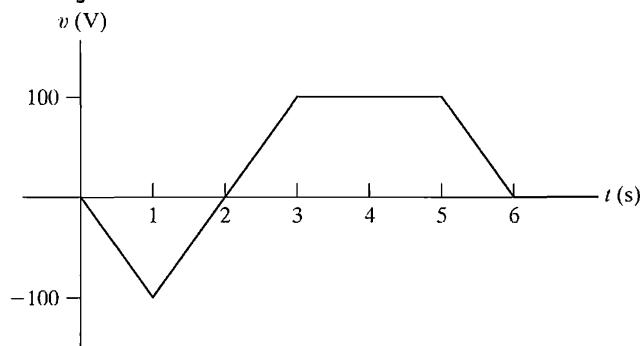**Figure P6.5****Section 6.2 Capacitors**


- 6.14** The current shown in Fig. P6.14 is applied to a  $0.25 \mu\text{F}$  capacitor. The initial voltage on the capacitor is zero.

- a) Find the charge on the capacitor at  $t = 15 \mu\text{s}$ .  
b) Find the voltage on the capacitor at  $t = 30 \mu\text{s}$ .  
c) How much energy is stored in the capacitor by this current?

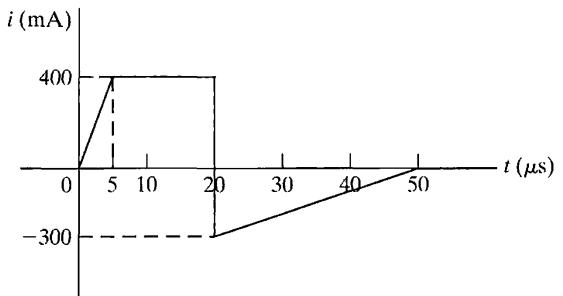**Figure P6.14**

- 6.16** The rectangular-shaped current pulse shown in Fig. P6.16 is applied to a  $0.1 \mu\text{F}$  capacitor. The initial voltage on the capacitor is a  $15 \text{ V}$  drop in the reference direction of the current. Derive the expression for the capacitor voltage for the time intervals in (a)-(d).

- a)  $0 \leq t \leq 10 \mu\text{s}$ ;  
b)  $10 \mu\text{s} \leq t \leq 20 \mu\text{s}$ ;  
c)  $20 \mu\text{s} \leq t \leq 40 \mu\text{s}$   
d)  $40 \mu\text{s} \leq t < \infty$   
e) Sketch  $v(t)$  over the interval  $-10 \mu\text{s} \leq t \leq 50 \mu\text{s}$ .

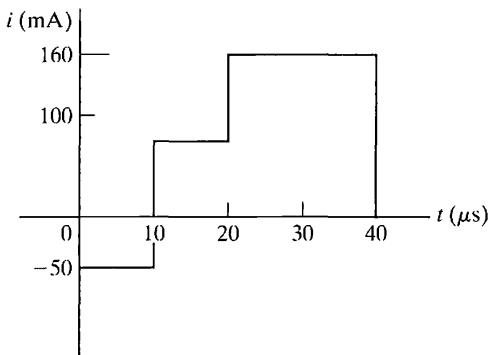**Figure P6.16**

- 6.17** A  $20 \mu\text{F}$  capacitor is subjected to a voltage pulse having a duration of  $1 \text{ s}$ . The pulse is described by the following equations:

$$v_c(t) = \begin{cases} 30t^2 \text{ V}, & 0 \leq t \leq 0.5 \text{ s}; \\ 30(t-1)^2 \text{ V}, & 0.5 \text{ s} \leq t \leq 1 \text{ s}; \\ 0 & \text{elsewhere.} \end{cases}$$

Sketch the current pulse that exists in the capacitor during the  $1 \text{ s}$  interval.

**Section 7.1 RL Circuits**

- 7.1** In the circuit in Fig. P7.1, the voltage and current expressions are


$$v = 160e^{-10t} \text{ V}, \quad t \geq 0^+;$$

$$i = 6.4e^{-10t} \text{ A}, \quad t \geq 0.$$

Find


- $R$ .
- $\tau$  (in milliseconds).
- $L$ .
- the initial energy stored in the inductor.
- the time (in milliseconds) it takes to dissipate 60% of the initial stored energy.

Figure P7.1

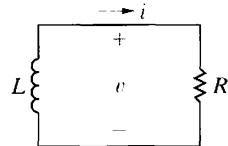


- 7.3** The switch in the circuit in Fig. P7.3 has been open for a long time. At  $t = 0$  the switch is closed.
- MULTISIM PSPICE
- Determine  $i_o(0^+)$  and  $i_o(\infty)$ .
  - Determine  $i_o(t)$  for  $t \geq 0^+$ .
  - How many milliseconds after the switch has been closed will the current in the switch equal 3 A?

Figure P7.3

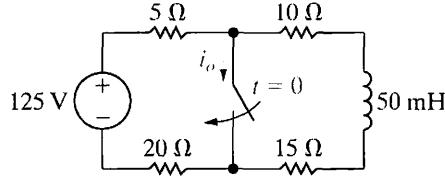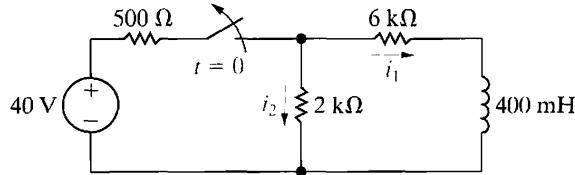

- 7.4** The switch in the circuit in Fig. P7.4 has been closed for a long time before opening at  $t = 0$ .
- MULTISIM PSPICE
- Find  $i_1(0^-)$  and  $i_2(0^-)$ .
  - Find  $i_1(0^+)$  and  $i_2(0^+)$ .
  - Find  $i_1(t)$  for  $t \geq 0$ .
  - Find  $i_2(t)$  for  $t \geq 0^+$ .
  - Explain why  $i_2(0^-) \neq i_2(0^+)$ .

Figure P7.4

**Section 7.2 RC Circuits**

- 7.21** In the circuit in Fig. P7.21 the voltage and current expressions are


$$v = 72e^{-500t} \text{ V}, \quad t \geq 0;$$

$$i = 9e^{-500t} \text{ mA}, \quad t \geq 0^+.$$

Find

- $R$ .
- $C$ .
- $\tau$  (in milliseconds).
- the initial energy stored in the capacitor.
- how many microseconds it takes to dissipate 68% of the initial energy stored in the capacitor.

Figure P7.21

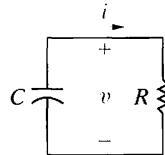

- 7.23** The switch in the circuit in Fig. P7.23 has been in position a for a long time and  $v_2 = 0$  V. At  $t = 0$ , the switch is thrown to position b. Calculate
- $i$ ,  $v_1$ , and  $v_2$  for  $t \geq 0^+$ .
  - the energy stored in the capacitor at  $t = 0$ .
  - the energy trapped in the circuit and the total energy dissipated in the  $25 \text{ k}\Omega$  resistor if the switch remains in position b indefinitely.

Figure P7.23

